

Frénic

8

W. H. T. ...

...

...

ADA 54 A


70 mm

Emulsion# 5-225-356-20

A
B
C
L
E
E
G
H
I
J
K
L
M
M
Y
O
P
Q
R
S
T
U
V
W
X
Y
Z


5/11/54 Obtained G-30-Computer, R.T. Unit, V.R. -
 Make up cables + control unit - checked at
 A.B. Radar -
 Fired Up + Checked wave forms
 Ran into trouble with leakage into C.A. scope
 + coax probe is next to useless
^{R.F. envelope}
 Wave form looked more reasonable when picked
 up With Hi-imp probe of 517 Tetrax, Sc.

Test Set-up as Follows

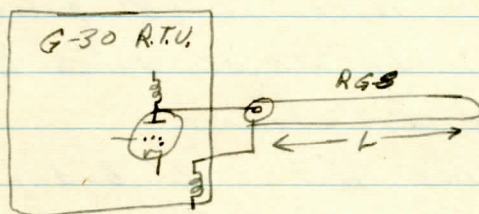

Run into all kinds of troubles in trying to view
 R.F. envelope -

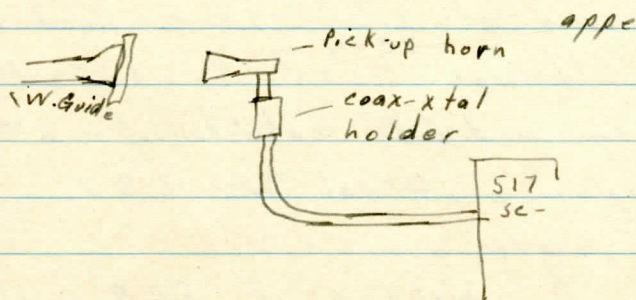Got some reasonable semblance of envelope
 with following set up - a lot of jitter but



$$\begin{array}{r} .26 \times 500 \\ .5 \\ \hline .130 \end{array}$$

For L of 36 ft. (RG-8U) γ should be

$$\frac{184 \text{ yds}/\mu\text{s}}{24 \text{ yds}} \cdot \frac{24 \text{ yds}}{184 \text{ yds}/\mu\text{s}} = .13 \mu\text{s}$$

By no manner or means can anything vaguely resembling a pulse envelope - some jizzle could be obtained with a horn pickup ant. However when using the Xtol. det. on the ant. coupler a neg + pos spike appear which appear to be associated with a wave form with steep rise & fall times - ~~when used~~ when checked against the $\frac{1}{2} \mu$ sec. pulse line it was .52 μs which checked with a current waveform from the pulse xfmr. - With 12 yd pulse line its duration (spike to spike) was .13 μs which checks precisely with computed duration -

Made pulse line with 15' (3 yds) of RG 58-U should have time of $\frac{2 \times 5}{184} = .0543 \mu\text{s}$

Measuring from ^{edge to} edge of ¹⁸⁴ jizzle From horn ant pickup + Xtol. det -

$$\begin{array}{r} \text{Vern } .93 \\ .37 \\ \hline .56 \text{ cm} \end{array} \quad .56 \text{ cm} \cdot \frac{1 \mu\text{s}}{184 \text{ cm}} = .056 \mu\text{s}$$

5 yd line

Photographed pulse at ^{1st exp} pulse xfmr. Used Hi-2 probe at J-110 - 517 scope 12KV $\frac{1}{30}$ s F3.5 PRF800

1st Shot⁰ swp - $\frac{1}{2} \mu\text{s}$ cm med. int. scale Full int - 2nd Exp same as first except it is of cal tr. 12.9 V


2nd Shot Same as above

3rd² " " " " with 12 yd RG 8 cable

4th³ " " " " " " " "

5th⁴

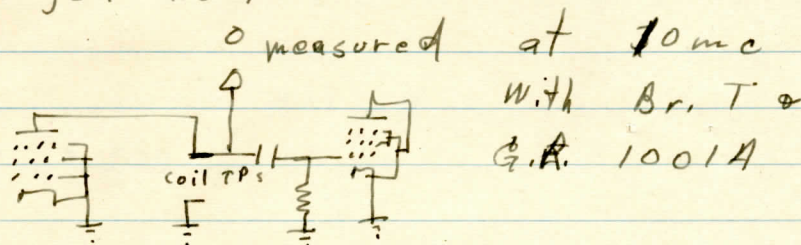5/12/54 Deter. interstage cop of 5702's
 chose two Raytheon 5702's at random
 & arranged as follow



R_1	$C_1 - 400 \mu\Omega$	$C_2 - 391.2 \mu\Omega$	C 8.8 $\mu\Omega$
R_2	$C_1 - 400$	$C_2 - 391.5$	8.5 $\mu\Omega$
R_3	$C - 400$	$C_2 - 391.8$	8.2 "
R_4	400	391.6	8.4 "
	400	391.4	8.6
		91.5	8.5 mean
			51.0 8.5 $\mu\Omega$

Two other tubes chosen at random

C_1 400 $\mu\Omega$	391.3	8.7	
	391.3	8.7	8.7 $\mu\Omega$
	391.3	8.7	

Two more tubes

C_1 400 $\mu\Omega$	391.3	8.7	
	391.2	8.8	8.7
	391.3	8.8	25.9 mean
			8.6

504
 50.4
 2016
 2500
 29016

2016
 25200

Laid out IF strip as follows

Wind coils

$$L_1 \quad 71.4 \text{ mc} \quad \text{---} \quad .584 \mu\text{H}$$

$$AC = 435 \mu\mu$$

$$L_2 \quad 60 \text{ mc} \quad \text{---} \quad .821 \mu\text{H}$$

$$AC = 309 \mu\mu$$

$$L_3 \quad 50.4 \quad \text{---} \quad 1.162 \mu\text{H}$$

$$AC = 218 \mu\mu$$

Wound 14 T. enam. # on ceramic core
with powdered iron slug - Wound $1\frac{1}{32}$ " long

with slug out

$$AC = 357$$

$$B = 370$$

$$L = \frac{1}{4\pi^2 f^2 C} = \frac{.712}{4.012} \mu\text{H} = .712 \mu\text{H}$$

$$Q = \frac{B}{G} = \frac{6.28 \times 357 \times 10^{14} \times 10^{14}}{22400 \mu\text{mho}} = 43.6$$

$$B = 6.28 \times 357 \times 10^7 \times 10^{-12} \times 10^6 = 4470 \mu\text{mho}$$

$$K = \frac{606}{43.6} Q = \frac{22400}{370} = 60.7$$

With slug in

$$\frac{604.5}{400} = 204.5$$

$$G = 370$$

$$Q = \frac{B}{G} = \boxed{34.7}$$

$$B = 6.28 \times 204.5 \times K = 12850$$

$$L = \frac{1}{39.4 \times 204.5} K = \boxed{\frac{1.28}{.800} \mu\text{H}}$$

Wound identical core with ^{13T} # enam. Wound $\frac{18}{64}$ " long

Slug out

$$AC = 331 \mu\mu \quad G = 291 \mu\text{mho}$$
$$B = K \times 6.28 \times 331 = 20800 \mu\text{mho} \quad Q = \frac{20800}{291} = \boxed{71.4}$$

$$L = K \frac{1}{39.4 \times 331} = \boxed{.766 \mu\text{H}}$$

Slug in -

$$AC = 167.3 \mu\mu \quad G = 155 \mu\text{mho} \quad Q = \frac{10430}{155} = \boxed{67.4}$$
$$B = K \times 6.28 \times 167.3 = 10430 \mu\text{mho}$$

$$L = \frac{1}{K \times 39.4 \times 167.3} = \boxed{1.519 \mu\text{H}}$$

Rechecked first coil - O.K.

Wound 2nd Coil same as above with 10T # enam.

Slug out -

$$c_1 = 856.8 \quad G = 405 \mu\text{mho}$$
$$c_1 = 400.0 \quad Q = \frac{28700}{405} = \boxed{70.8}$$

$$AC = 456.8 \mu\mu$$

$$B = K \times 6.28 \times 456.8 = 28700 \mu\text{mho}$$

$$L = K \frac{1}{39.4 \times 456.8} = \boxed{557 \mu\text{H}}$$

Slug in -

$$a_1 = 635.4 \quad G = 197.5 \mu\text{mho} \quad Q = \frac{14790}{197.5} = 74.9$$
$$c_1 = 400.0$$
$$AC = 235.4 \mu\mu$$

$$B = K \times 6.28 \times 235.4 = 14790 \mu\text{mho}$$

$$L = \frac{1}{K \times 39.4 \times 235.4} = \boxed{1.001 \mu\text{H}}$$

Wind L with 8 T # enam.

Slug out

$$\begin{array}{r} C_2 - 1075.9 \\ C_1 - 400.0 \end{array}$$

$$G = 670 \mu\text{mhos}, Q = \frac{42500}{670} = \boxed{63.4}$$

$$AC = 675.9 \mu\text{V}$$

$$B = K 6.28 \times 675.9 = 42500 \mu\text{mhos.}$$

$$L = \frac{1}{K \times 39.4 \times 676} = \boxed{.376 \mu\text{H}} \text{ min.}$$

Slug in

$$\begin{array}{r} C_2 - 749.2 \\ C_1 - 1075.9 \end{array}$$

$$G = 300 \mu\text{mho.}, Q = \frac{21900}{300} = \boxed{73.1}$$

$$C_1 - 400.0$$


$$AC = 349.2 \mu\text{V}$$

$$B = K 349.2 \times 6.28 = 21900$$


$$L = \frac{1}{K \times 39.4 \times 349.2} = \boxed{.727 \mu\text{H}} \text{ max.}$$

Monday-

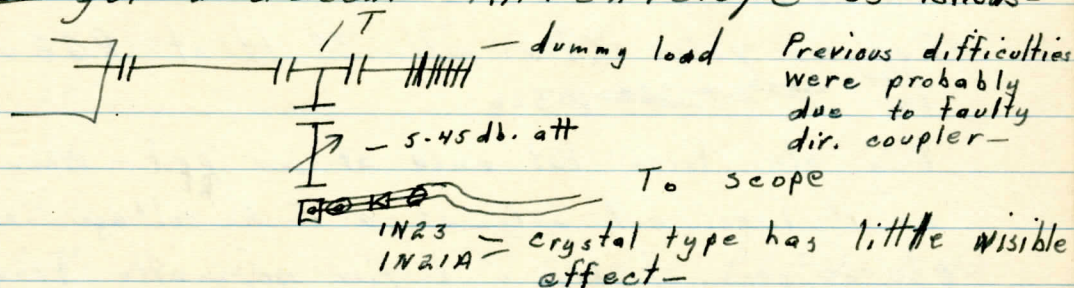Obtained more microwave gear and ~~at~~ got a decent R.F. envelope as follows-



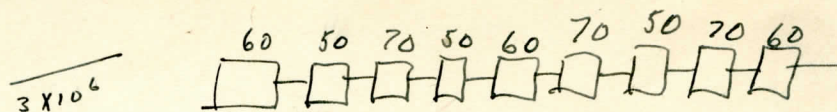With set of 15' of RG58 (for pulse line) maggie firing becomes erratic + critical. It would with some Fiddling around fire with a good bit of jitter on the trailing edge - ~~the~~ $T_{\text{was}} \approx .02 \mu\text{s}$



Make Osgr. of Voltage + current of Maggio
→ r.f. pulse

Voltage = 2 K.V.


5th #4 1st Exp 24 KV Full ret brill F-3.5 $\frac{1}{30}$ sec SWP 100 μ s/cm

R.F. envelope Xtal det. thru T + 40 db. att- ^{input 20 Ω} scope = 170 Ω

2nd Volt tr. ^{.14V} ret. Full brill $\frac{1}{30}$

6th #5 1st 24 KV same as 5th ~~X~~ ^{Hiimp 2 probe} swp 100 μ s/cm

2nd Volt tr 11.8 V

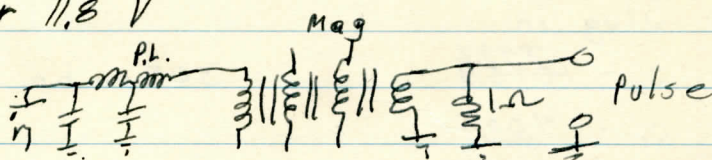

7th #6 Exp Same as 5th Except for swp. of 200 μ s/cm
to Volt calib .13 V.

8th #7 Exp Same as #6 13V calib + 200 μ s/cm swp

With .5 μ s. pulse center Freq. was
on Microline Fr. M. 3.5-11.6 ^{MHz}

Mag. fired normally throughout range ~~had firing~~ ^{prf}
with no jiller-

Replaced pulse Xfmr. with 30 Ft of RG8U cable
⁶²⁰ 184 = ~~4.32~~ ~~3.26~~ .0326

Mag still Fires but only at low ^{prf} - When first switched
on it fires but only at a 5 db voltage loss - after
30-60 secs. it begins to fire normally Freq ¹⁵ was 3.5-12
No apparent mistfiring pulse is .09 μ s long

9th Photo #8 Same as 5 except for 50 μ s/cm. swp. .19 V cal

10th " #9 Same as #6 " " " " 10.4V

11th #10 Same as #9 ex. 100 μ s/cm - .2V cal

12th Ph. #11 Mag. cur. pulse 200 μ s/cm 10.8 V cal,

13th " 12 " " " " " " " "

Reduced pulse line to 25 ft. Mag Fired as before except for less jitter pulse was 2.08 μ s long Freq. remained the same -

14th Photo 13 Same as 5th except for 20 μ V/cm swp. + .11 V. cal

15th " 14 " " " " 50 " " " "

16th " 15 " " 6th " " 20 " " 8.7 " "

removed 3rd line 17th " 16 " " " " " 50 " " " "

18th " 17 " " " " " 200 " " " "

19th " 18 " " 5th " " 20 No cal tr

20th " 19 " " " " " 50 " " "

21st " 20 " " " " " 100 " " "

22th Removed 3 ft of line + there was little change in operation of mag - slight jitter appeared on leading edge of pulse - freq remained the same - appreciably more FM shown by Freq. meter. reduced 3 ft more + only slightly more jitter + FM. same freq.

22 " 21 same as 5 - 50 μ V/cm sw no cal

23 " 22 " " " 20 " " " "

24 " 23 " " " 100 " " " "

25 " 24

Reduced line by 3 ft more - PAF had to be raised to get Mag to Fire (Variations in waveform at Thyatron?) looked fair relatively small amount of jitter

2) exp 26 " 25 " " " 20 " " "

27 " 26 " " " " " "

28 " 27 " " " 50 " "

Cut off 3 more ft. jitter ~~peak~~ peak per red.
29 28 same as 5 sweep ^{20 mV/cm} No cal
" Took off 3 more ft + Mag would not fire

Test F-1.5 lens on M-1 Osc. camera
Fed in 50 mc wave from GR 1021 P3 Gen.

$$\frac{4 \text{ in} \times 2.5 \text{ cm}}{3 \text{ us}} = \frac{10 \text{ cm}}{3 \text{ us}} = 3.33 \text{ cm/us} \text{ or } \frac{3}{10} \text{ us cm}$$

Almost max. brill 24 KV ~~Run~~ swp. 5 us/cm 800 vprf
F 1.5 FD = $13 \frac{5}{8}$ " XX film. Ran O.K.
2nd Run same but with swp of 2 us/cm
Ran O.K.

Monday


Supply - 1X2 Hi Volt rect - 6BQ6-6CU6 Flyback Xfmr.
check on Holcher + C.R.T.3

Have 2.75" reflector built + rocket model built

Get Camera ready for inst -

5/19/54

Work on IF strip

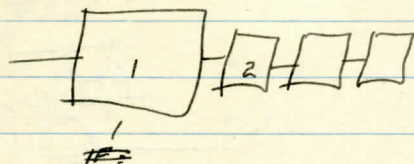

Ch. V. at

Aligned to

+ 7.95 1.25	1 - 50 to 72. Mc	60 MC
+ 1.85 1.72	2 - 60 to 83 "	70 "
+ 1.95 1.8	3 - 38.2 to 55 "	50 "
+ 1.80 2.7	4 - 48.1 to 85 "	71 60 "
+ 1.80 1.9	5 - 48.0 to 68 "	60 50 "
1.92	6 - 42.5 to 59 "	50 70 "
1.8	7 - 65 to 91 "	71 71 "
1.65	8 - 58 to 40.5 "	50 "
1.75	9 - 50 to 70 "	60 "

Check Sens & Align.

Measure D.C. voltage at Det. - See reverse page for CK

Used 1001-A GR Gen. & H.P. 608A - H.P.'s Voltage


Calib. is obviously wrong - ~~reads~~^{is} very low -

assumed it was flat however & took initial calib.

From 1001-A -



IF Strip is touchy on B+ decoupling - has $\approx \pm 5$ V. noise
at last 4/c kkt. observed on 517 test. scope -

Feed Signal in as follows -

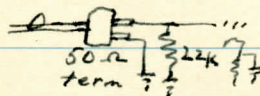

$$R_L = \frac{6.3 \times 10^3}{.05 \times 10^7} = 50 \Omega$$

identical
triples

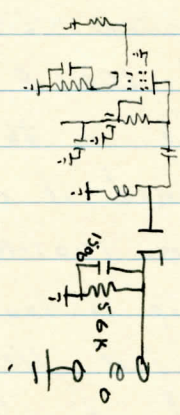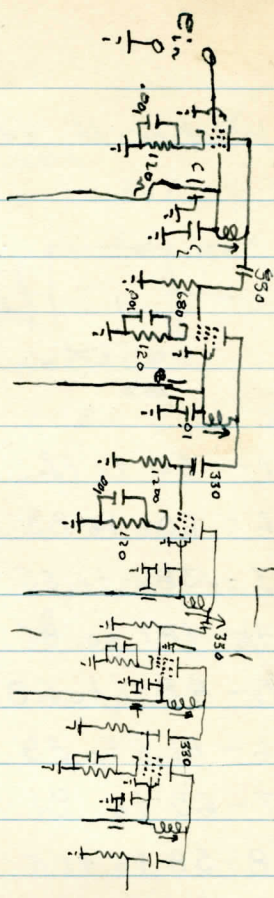

Shot noise puts bias of +.75 volt on e_o

e_{in}	e_o	Freq	G
$.4 \times 10^{-3}$	+1.0	50 mc	
.85 "	+1.5	50 mc	
2.1 "	+2.5	50 mc	
3.0 "	+3.0	50 mc	
4.5 10 "	4.0	50 mc	
14 "	5.0	50 mc	
18	6.0	50 mc	


Held e_o at + ~~4.5~~ 1.

e_{in}	F mc	e_{in}	F mc
210			
425	50 mc	200	72
500	45.6	370	74
1000			
425	46.0	500	75
260	47.0		78
180	48.0		80
130	49.		
100	50		
80	52		
78	54		
70	56		
62	58		
62	60		
55	62		
60	64		
60	66		
80	68		
110	70		

Parts - .01 ceramic cond.
Wire + resistors for R.F. chokes


$$\frac{Z_1}{Z_2} = \frac{T_1^2}{T_2^2} \quad \frac{1080}{300} = \frac{171}{36} \quad \frac{36,399}{1096}$$
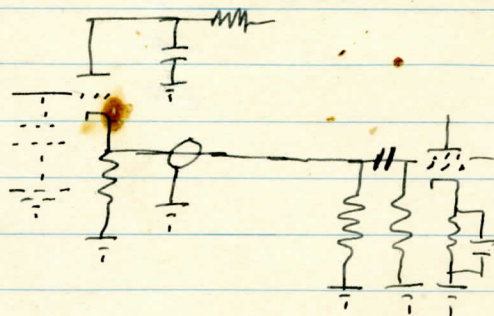
$$\text{Rise time} = 2.2 RC = 2.2 \times 5 \times 10^{-12} \times 10^3 = 5 \times 10^{-9}$$



$$\begin{array}{r} 4 \\ 4 \\ \hline 16 \\ .07 \\ \hline .07 \overline{) 1600} \\ 100 \times 3 \\ \hline 3 \\ 100 \end{array}$$

Det. Freq. Respon. of C.F.

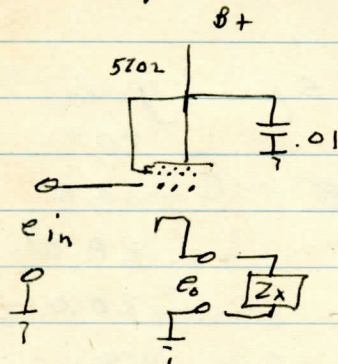

Case 1. Connected 3' of RG-55 U across e_o
had 11 db loss at 50 mc
Had some loss at 15 mc

$r_p = \frac{A_{ep}}{A_{ip}}$ Theor. loss using 5703

$$\frac{20}{3.8 \times 10^{-2}}$$

$$\approx 5 \times 10^3$$

$$\gamma = \frac{\mu R_k}{r_p + (1 + \mu) R_k} = \frac{25(75)}{5 \times 10^3 + (26)75} = \frac{1950}{7000} \approx \frac{2}{7} = .29$$


≈ 11 db loss.

$$\frac{2}{7} = 3.5$$

$$\frac{.545}{20} = 10000$$

$$\begin{array}{r} 12.2 \\ 8.5 \\ 38 \\ \hline 25 \\ 26 \\ 50 \\ \hline 100 \\ 1950 \\ 5000 \\ 6950 \end{array}$$

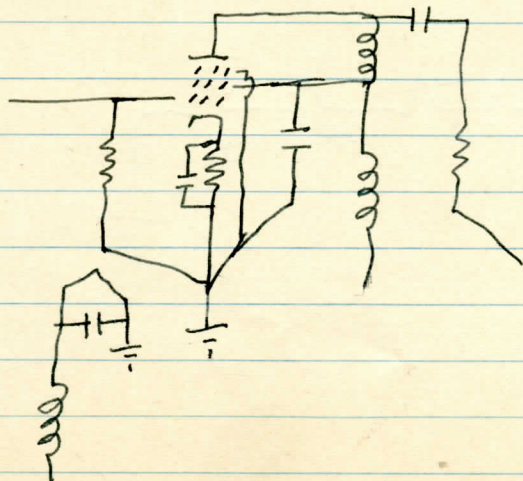Try to salv. i.f. built on Cu-strip
Change grounds, Improve decoupling & shielding



Allow for grid loading

51. Determine Freq. Resp. of M-1 A-scope

100 μ A gen

eg

Freq.

e_{in}

~~e_g~~

e_p

gain

.150

|

~~1V~~

~~4V 3V~~

40X

.5

|

~~2.3~~ 1.78

35.5

1.0

|

- 1.78

28.0

1.5

|

- 1.78

20.0

2.0

|

14.

~~2.5~~

|

1.99

~~8.9~~

3.0

|

- 2.24

8.9

~~4.5~~

|

- 2.5X

5. X

4.0

|

4.5


|

5.0

|

10

- 4.4

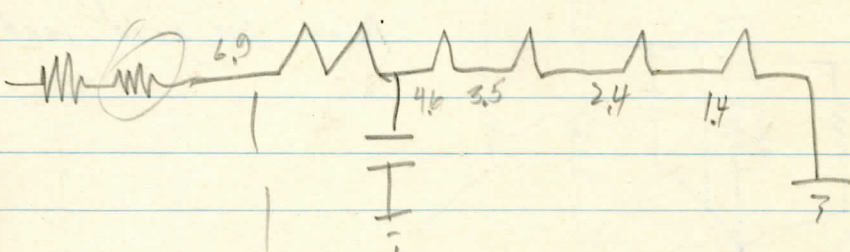

5/23/54

Run more test on osc. camera.

$$\frac{4 \text{ in}}{3 \text{ usec}} \times 2.5 \text{ cm/in} = \frac{10 \text{ cm}}{3 \text{ usec}} = 3.3 \text{ cm/usec}$$

3.3 $\overline{)10.0}$

or .30 usec/cm - 2 usec/cm swp
~~the~~ highest possible intensity with
which focus could be maintained
+24 KV acc-


Shot First roll at F-16

" 2nd " " F-1.5


F.D. 12" Varied from 8" to
16" & then held steady

Forgot to turn on trace
so ran again same way
also ran #1 over

Test of 25 mc 1F Amp

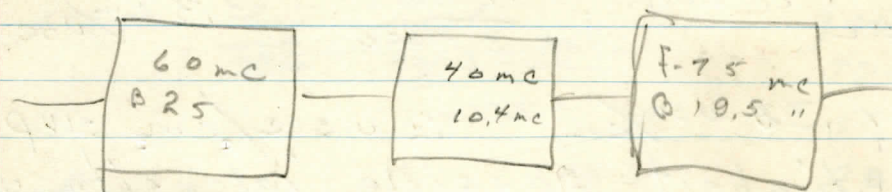

detection method -

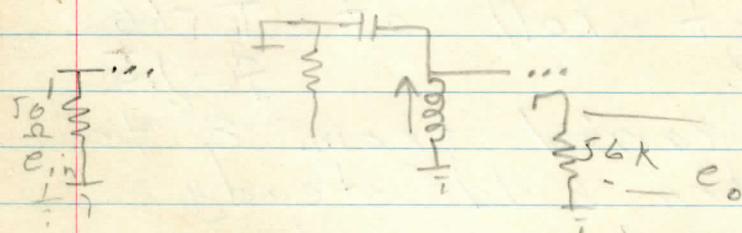

at output of 1st 3X const d.c. of +38V
at C_0 - B+ @ 120 Ip = 44 ma.


F	c ₁	c ₀	G
60	.04	1	$\frac{.04 \times 25}{1.00}$
75	.14	1	7.1

thru 2nd triple


steady .46V

120 @ 90ma

F	c ₁	c ₀	G
60	.002	1	$\frac{.002 \times 500}{1.000}$
75	.01	1	100
70	.007	1	142

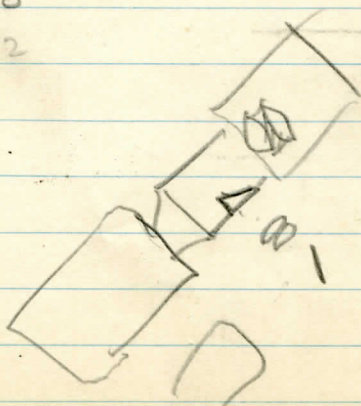

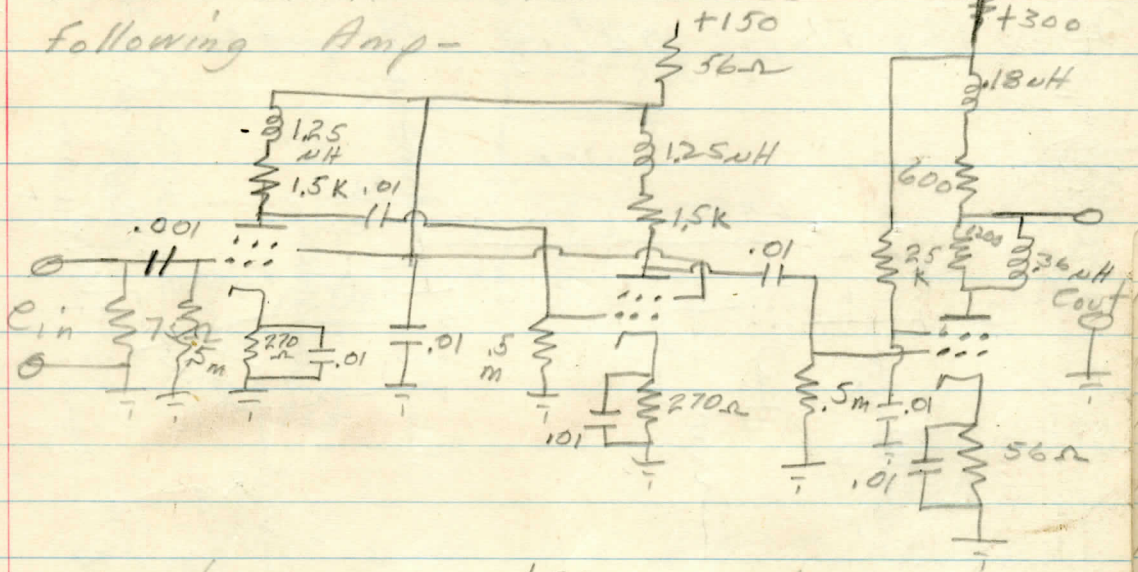Build & Check Characteristics of
Following Amp -



$$X_c = \frac{L}{6.3 \times .01 \times 10^{-6}} = \frac{1.00}{.06} = 16 \times 10^6 \times f$$

.01 ceramic

56 ohm - 68 ohm


600 ohm 25K ohm 2W

$$X_L = 10 \text{ m}\Omega \quad L = \frac{1}{4\pi^2 f^2 C}$$


$$C_1 = \frac{1}{39.4 \times 10^{14} \times 1.25 \times 10^{-6}} = \frac{1}{49.2 \times 10^{16} \times 10^{-6}} = 2.015 \times 10^{-10}$$

$$C_2 = \frac{1}{49.2 \times 10^{12}} = 2.015 \times 10^{-5} = 20.15 \text{ nF}$$
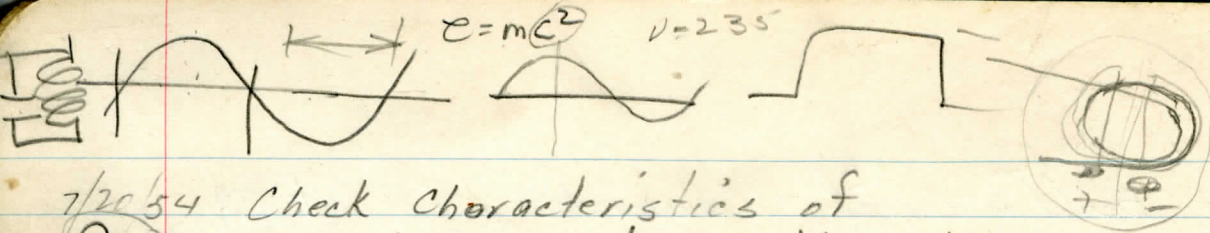
$$C_2 = \frac{1}{49.2 \times 10^{-6} \times 10^{16}} = 2$$



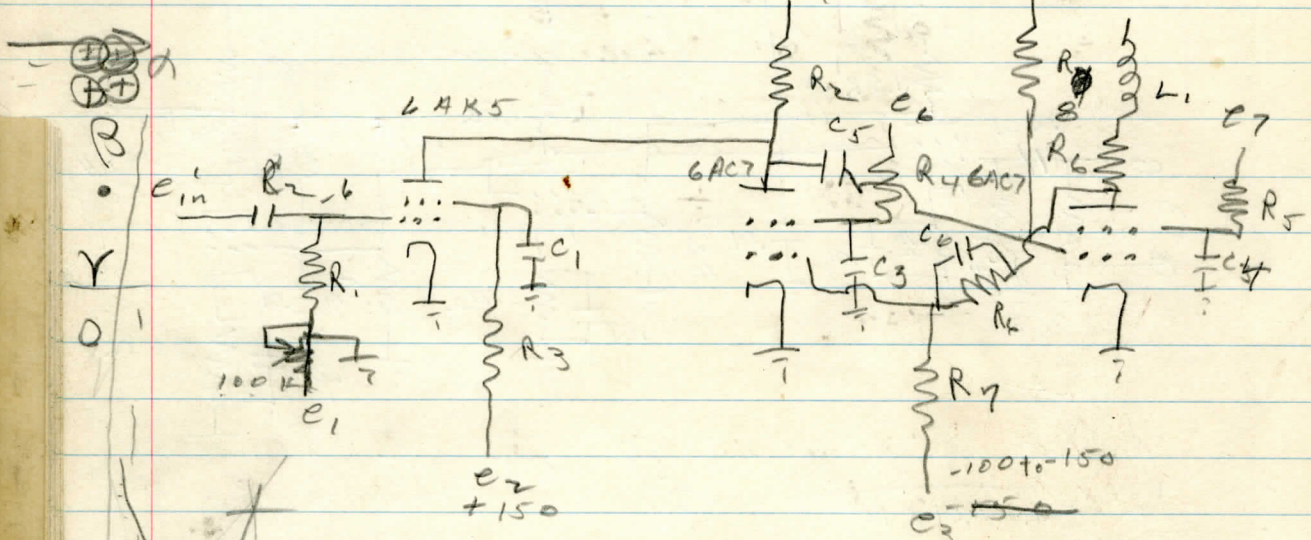7/20/54 Check characteristics of
Flip Flops gating ckt's etc.



- $R_3 - 200K$
- $R_1 - 200K$ $C_2 - 50\mu F$
- $R_2 - 10K 1W$ $C_3 C_4 - .01$
- $R_6 - 15K 4W$ $C_6 - 50\mu F$
- $R_7 - 120K \frac{1}{2}$ $R_{7-4} = 7.5$
- $R_6 - 150K \frac{1}{2}$
- $R_{4-5} 7.5K 1$
- $R_8 - 120K 1W$

$$\frac{10^2}{4.5 \times 10^3} = 2.2 \times 10^{-2}$$

$$\frac{7 \times 10^3}{3 \times 10^3} = 2.3 \times 10^{-2}$$


$$2.2 \times 10^{-2} \times 230 = 5.06$$

$$2.3 \times 10^{-2} \times 230 = 5.29$$


Looks good - starts in 50 msec

draws $B+150 - 5ma$ $B+300 - 15ma$
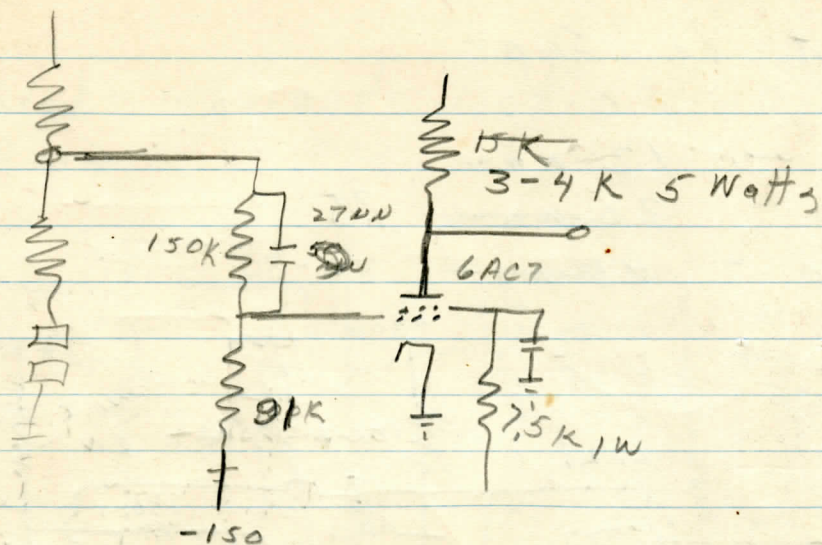
$$6AC7 - 10 \times 10^3 \times \frac{2.3 \times 10^2}{1.8 \times 10^4} = 12.8ma$$




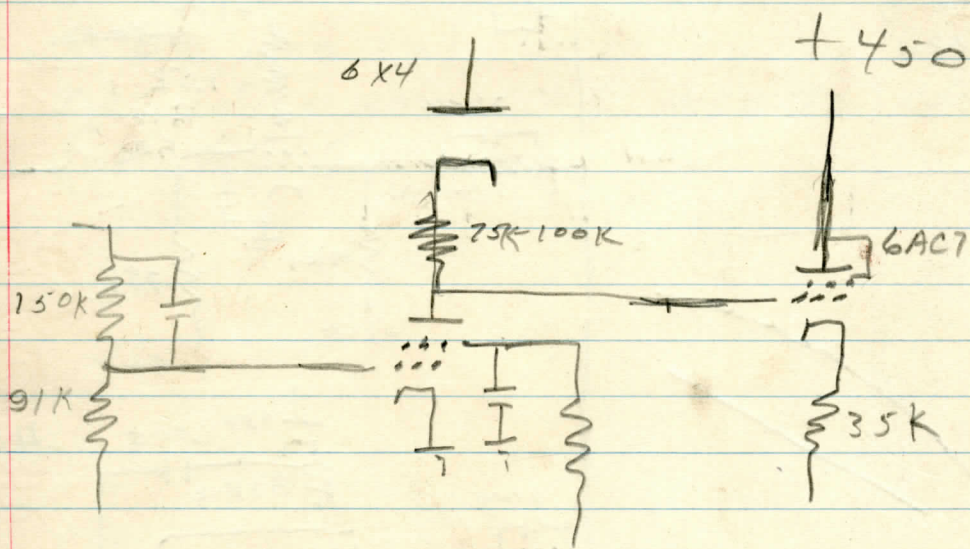Use 6AG7 slightly above 6AC7 ratings
looks good




Input to 5wp-

-150 - 12 mo-
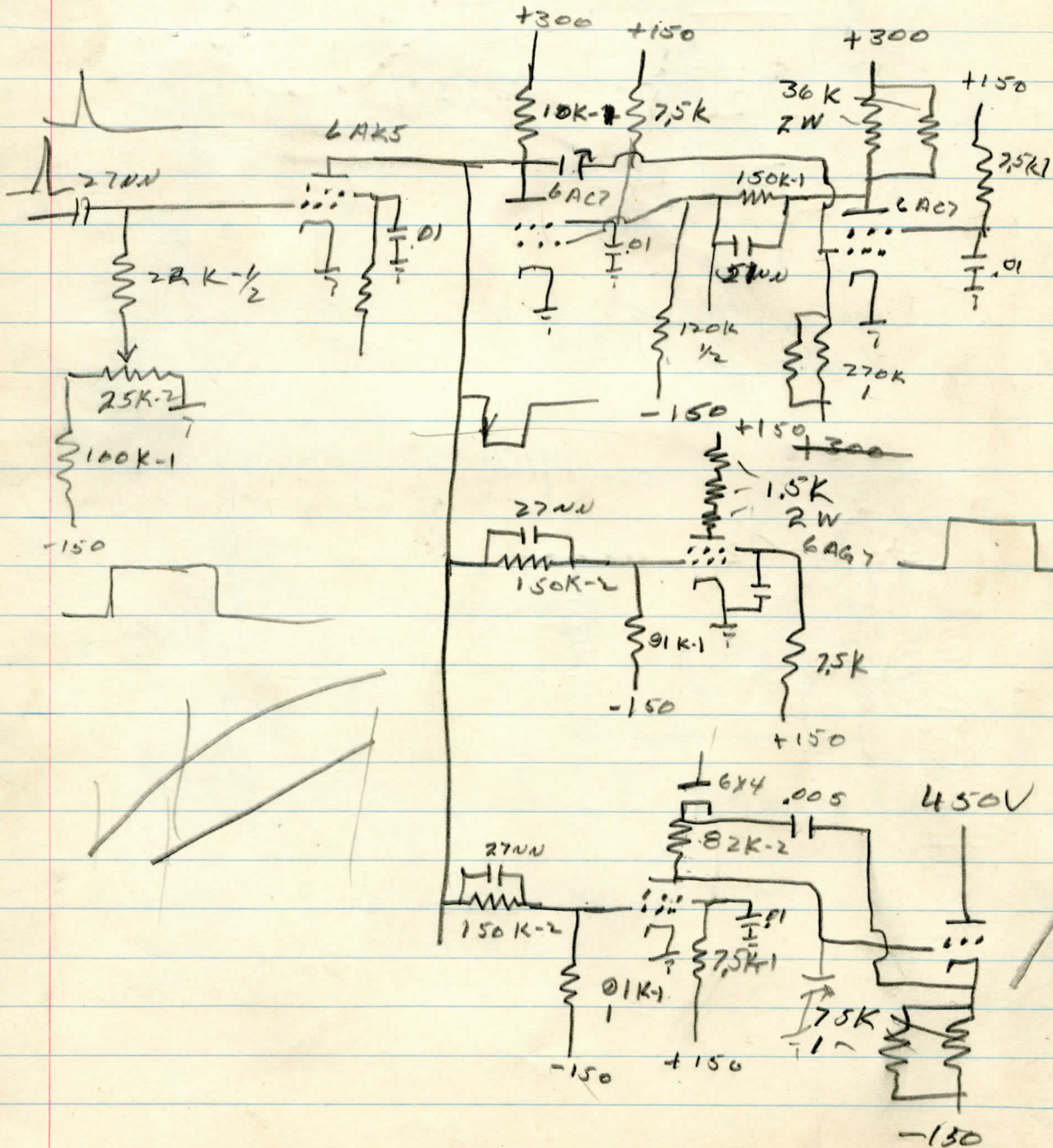
$$+150 - 20 \text{ mg} - 25$$
$$+300 - 45 \text{ ma} - 30-35$$

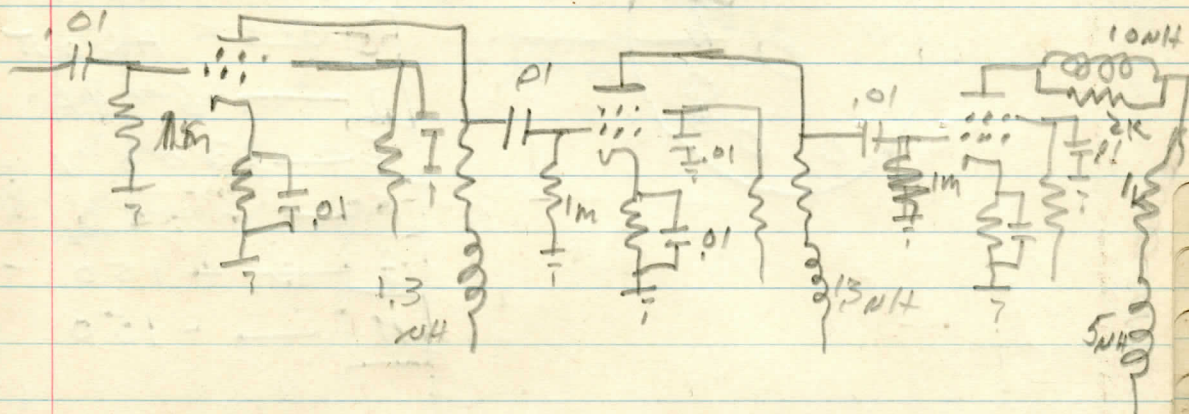
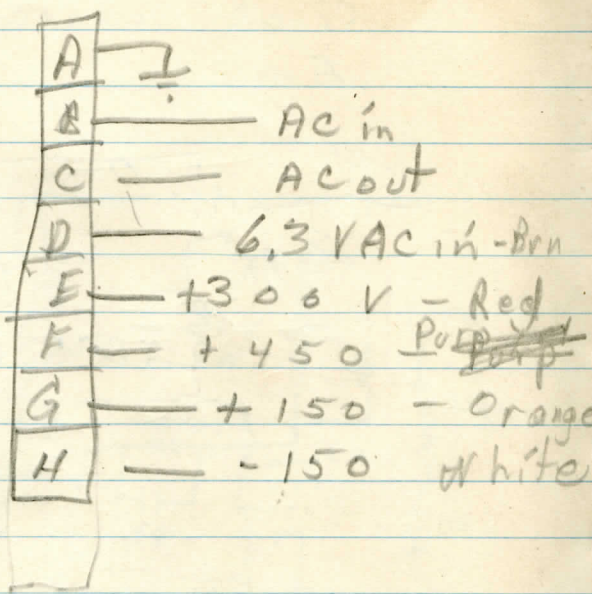
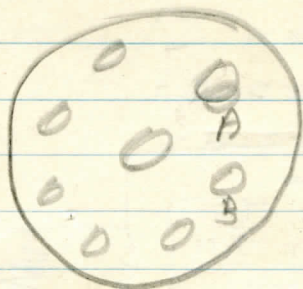
check characteristics of this
Amp




5 μ H coil - 3 meg ohmite 1W res
scramble wound with 40T
#28 enamel

5 μ H coil - same as above except
for 62 Turns.


Inter connections






300
250

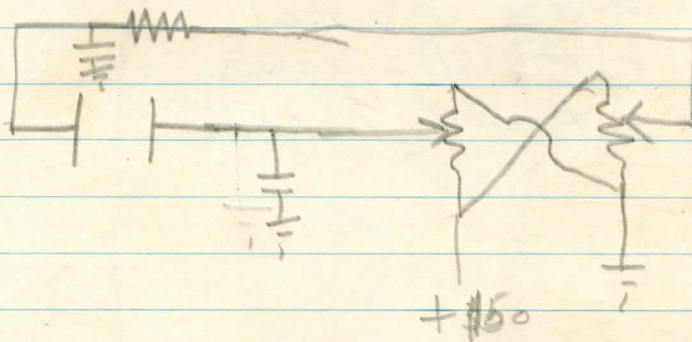

B Sweep & Video For M26 A scope

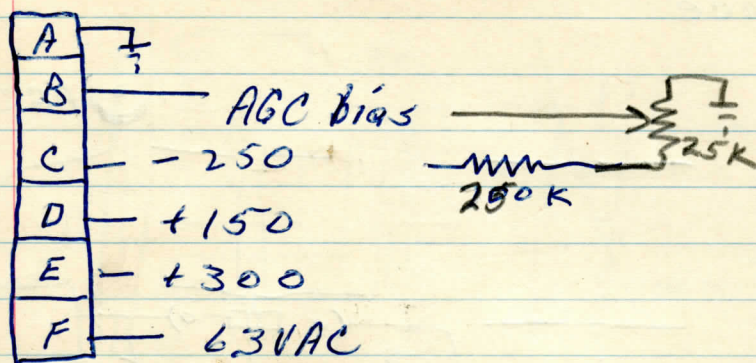

7/20 servo for positing solar furnace

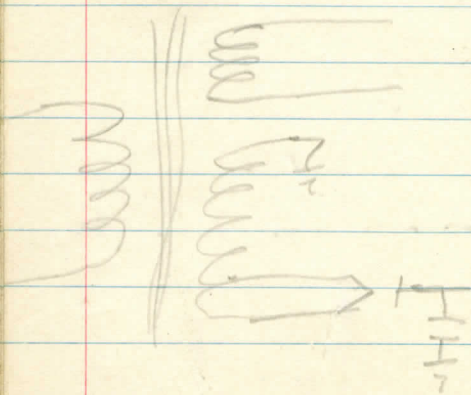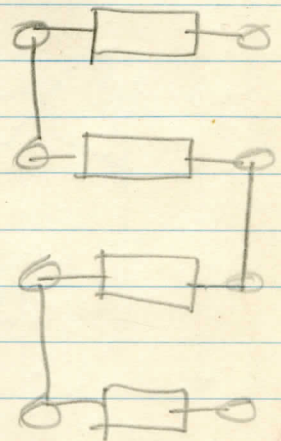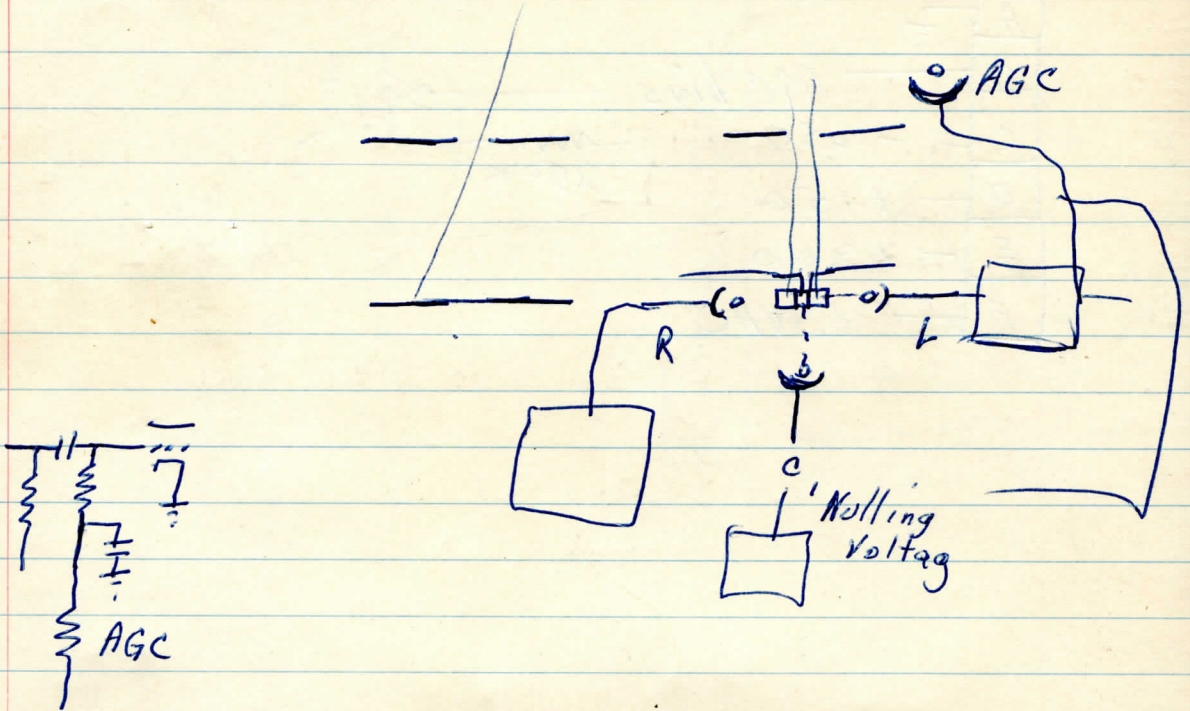

7/31

Roll - 1A

Photos For Canada

M26 R.O. F.F.I.


Swp - B -

all traces 12KV 30F4

- | # | Description | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
|-----|------------------|------|---|---|---|---|---|---|---|---|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|
| #0 | Input to trig | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
| #1 | Plate of multi | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
| #2 | " " " | 2.5 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
| #3 | " " " | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
| #4 | grids of gates | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
| #5 | " " " | 2.5 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
| #6 | Gate to CR | 2.5 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
| #7 | " " " | 12.5 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
| #8 | Neg sweep | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
| #9 | " " " | 2.5 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
| #10 | Pos " " | 2.5 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
| #11 | spoiled | | | | | | | | | | | | | | | | | | | | | | | | | |
| #12 | Pos. SW. | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
| #13 | Pos. Pl. of FF | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
| #14 | " " " | 2.5 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
| #15 | Neg grid of F.F. | 2.5 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
| #16 | " " " | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
| #17 | Pos " " | 2.5 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
| #18 | Neg Pl of " " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " |
| #19 | " " " " | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
| #20 | Neg Grid " " | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
| #21 | " " " " | 2.5 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
| #22 | Pos " " " | 2 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
| #23 | " " " " | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
| #24 | Video grid | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |
| #25 | " Pl | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 |

~~Remove~~

Left only V-615 & V-614
in R computer

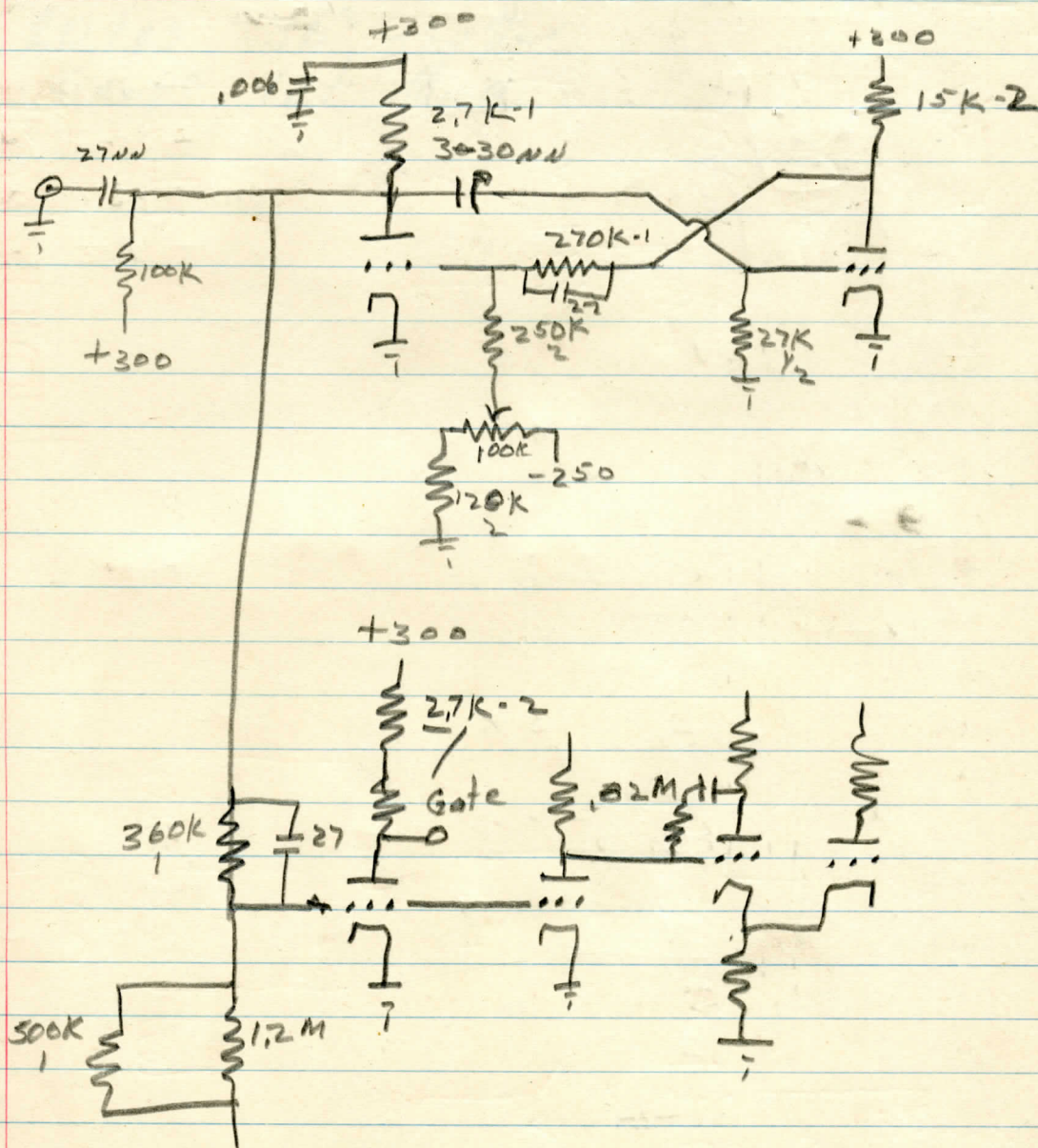


8/1/54

Test flt. of M26 Tank BB G

F - 11 Cl. A
20fps 36° shutter
Scope Int Med

30 ne kontr -


4.4 ppts 40m

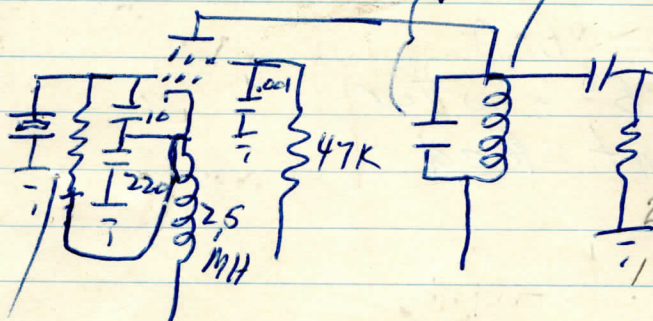
 $- 2.5 \mu A$ 



+ 450 ~ 30mg


$$25 \text{ N} + 300 \text{ N} \approx 50 \text{ N}$$
$$120N + 150 \approx 25$$

5 - 250 - 25

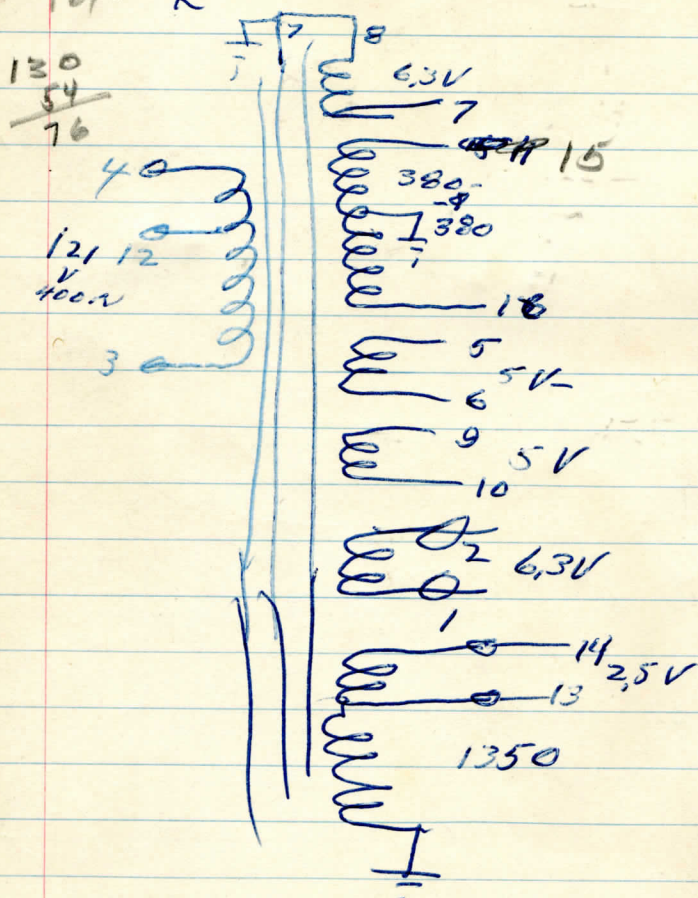

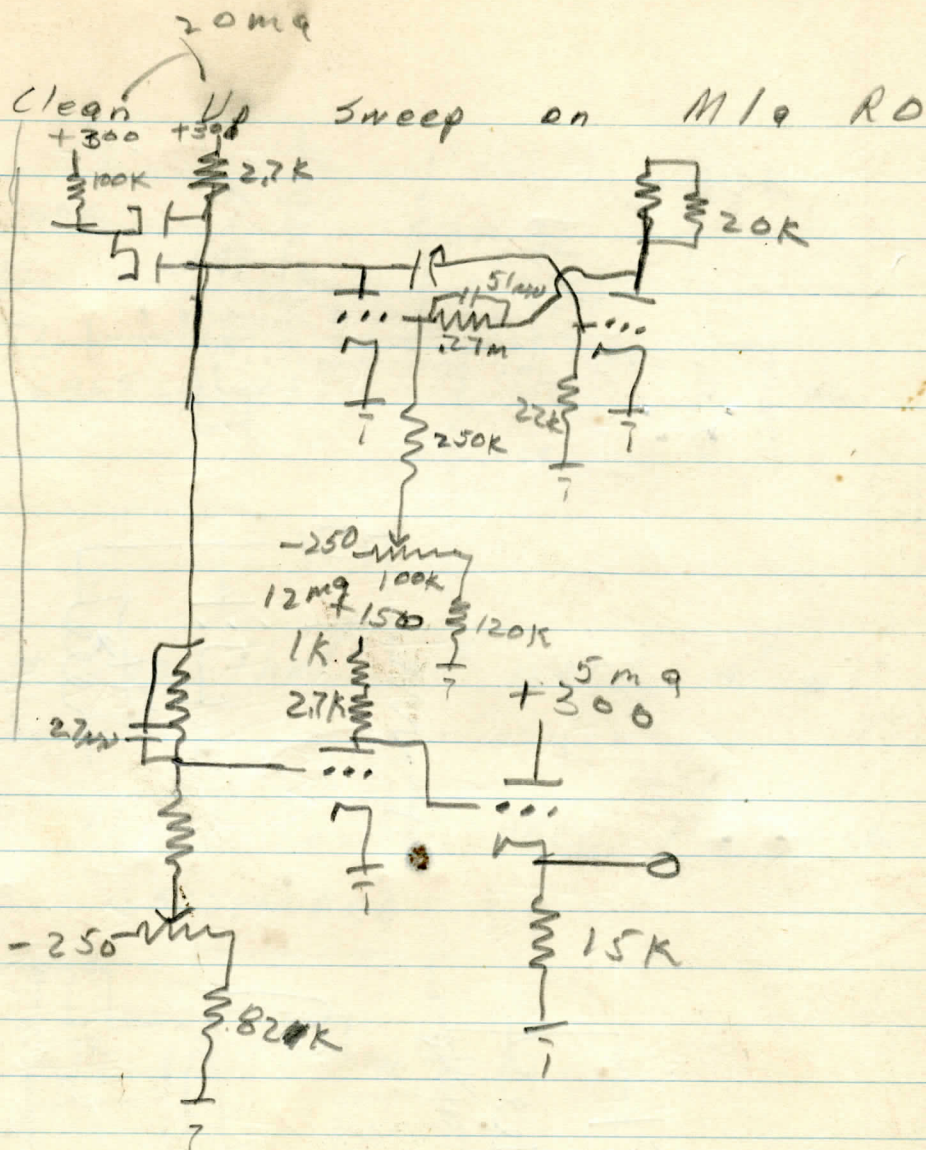


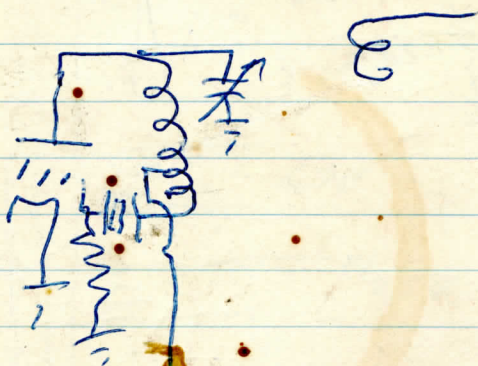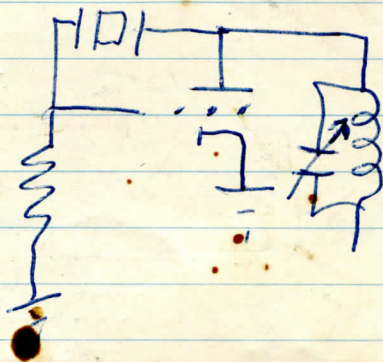

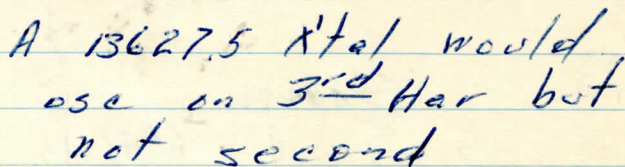



Tried 27.255 & 13.6275
K'tals, in all these ckt's
under various conditions
but none would take off

also tried these

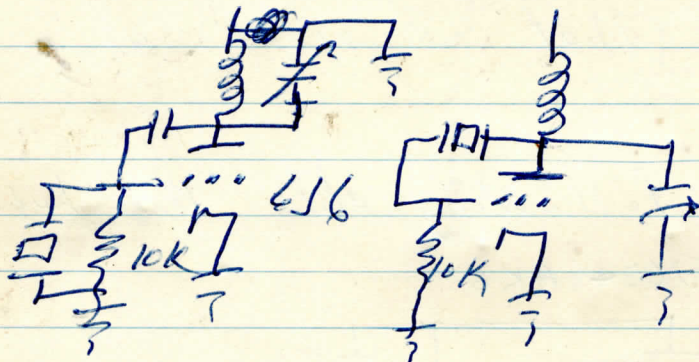

try this - No luck

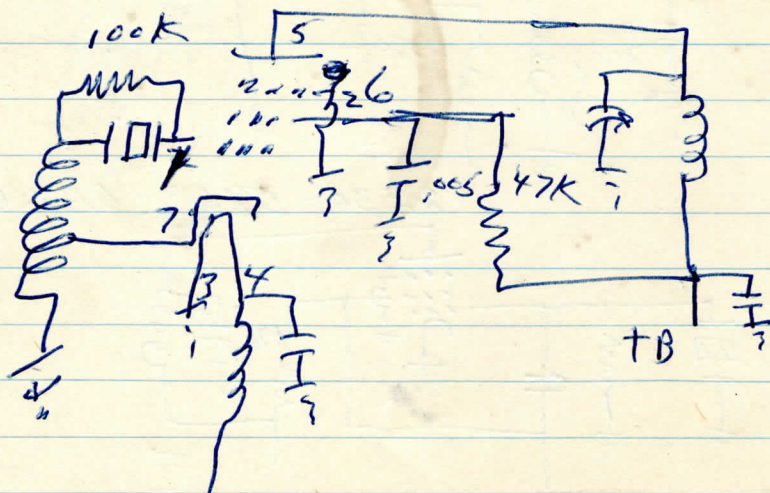
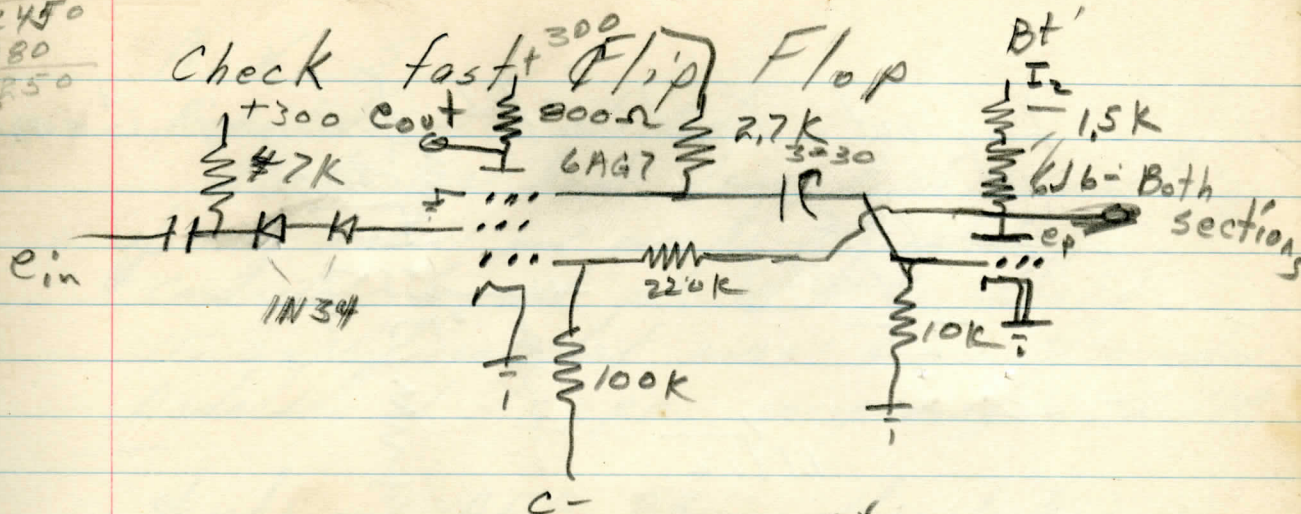
$$\begin{array}{r} 490 \\ + 1025 \\ \hline 2450 \\ + 980 \\ \hline 12250 \end{array}$$


Good Ckt. $e_q = 125V$
 with $B+ = 300V$ I_2 is $40mA$
 " " $= 150V$ I_2 " 17 "

with $B + = 300$ I_2 is 40 mA
" " = 150 I_2 " 17 "

$$= 150, \bar{I}_2 \quad " \quad 17 "$$

Current drawn by 300V is
negl. ≈ 1 mA.

Minimum pulse length $\approx 3 \mu\text{sec}$

1.25

1020

2.5 #0

Roll #	Film	Exposure	Time	Sec	Swp	100 nuss/cm	V	B+
								300V
F-8	T-1	sec	swp	100	nuss/cm	V=115V	cm	
"	2	"	"	"	"	V=		
"	1	"	"	200	"	V=100V	B+=150V	
"	2	"	"	"	"	"	"	
"	1	"	"	100	"	"	"	
"	2	"	"	100	"	"	"	


$$B_+' = 300V$$
$$V = 115 \text{ V cm}$$
 $V =$

200" $V = 100V$ $B^+ = 150V$

4

$-6 \overline{) 4.15}$

$$1.1 \sqrt[4]{12}$$

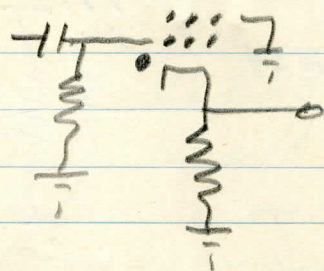

Build 20 KV hi volt supply
" low " "

Build 20 KV hi volt supply
" low " "

Love

—

200

$\begin{array}{r} 2 \\ 2 \\ 4 \\ 2 \end{array}$

$\begin{array}{r} .16 \\ .16 \\ .96 \\ .16 \end{array}$

$\begin{array}{r} 256 \\ 18 \end{array}$

$\begin{array}{r} 256 \\ 32 \\ 530 \\ 18 \\ 50 \end{array}$

$\begin{array}{r} 464 \\ 58 \end{array}$

$\begin{array}{r} 10,44 \end{array}$

$\begin{array}{r} 1.8 \\ 1.8 \\ 784 \end{array}$

$\begin{array}{r} 1.8 \\ 1.1 \end{array}$

$\begin{array}{r} 1.8 \\ 1.8 \end{array}$

Noe

B

No 3


Reported in & started.

Electronics had done little or nothing of any value on work requested. Contacted Garret at R & C about I.F. amplifiers that were a month overdue. Ordered scope comp. of SCR 718

1. Run test on horn antenna
2. Observe ^{+ photograph} waveforms as follows:
R.F. envelope and spectrum.
Mazzy voltage and current.
Targets from detectors


R.F. envelope ^{Mag} Current + Volt Tgts

R.F. envelope

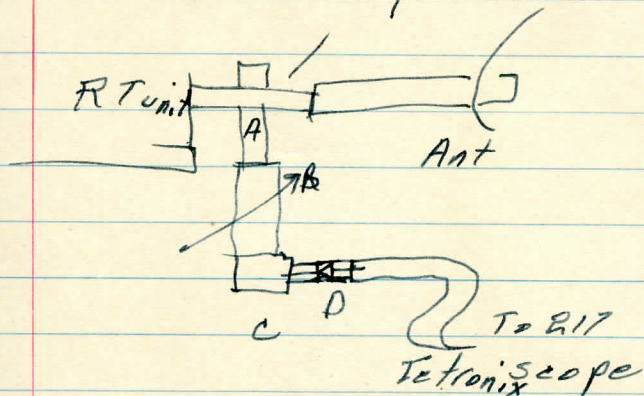

Wouldnt work
bad Adapt (C)

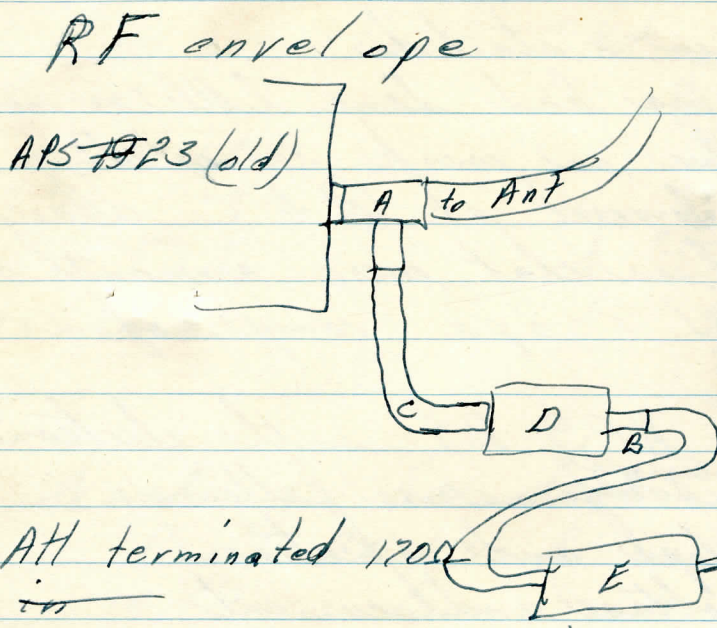A directional couple
20db loss
Sperry #235
B-Var Att.
Sperry Ant 134
C-Waveguide to
Coax adapt.
Sperry 167 A
D-detector
Coax with
1N23 xtal.



A - sperry T
165 A

D - sperry ATT
M #134 A

C - flex X band
waveguide

B - coax detector

E - Tetronix ATT

F - " scope

RF spectrum

.25 nsec/cm

R.F. ATT

Vid. ATT

Exp 0 -

"

45 db

23 db

Volt across 1 -

"

"

"

Fil of 2 -

"


58 db

Mag 3 -

"

"

Magnetron voltage wave shapes

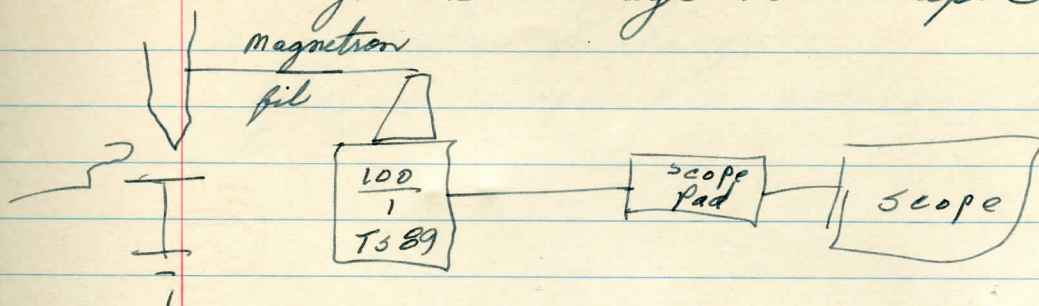


Problem: Simple yet accurate range
determination of targets.

Use J scope for accuracy and ^{delayed} trigger
to

$$dB = 20 \log \frac{V_1}{V_2} = 20 \log 10^4$$

Nov 20 '54 Test i.f. strips -

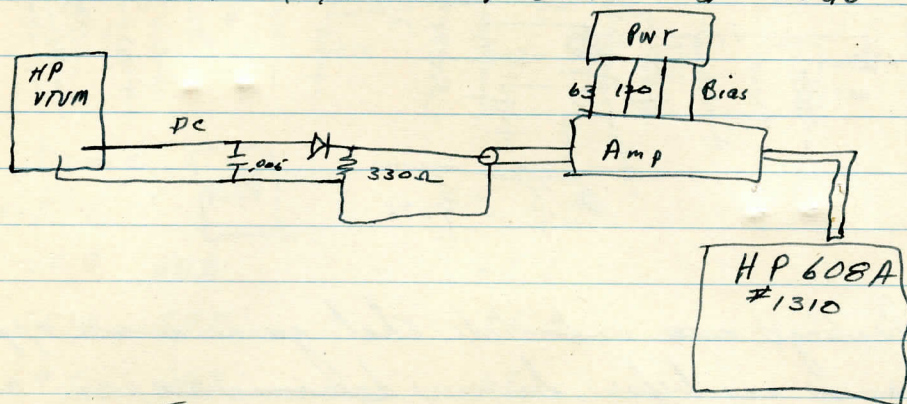50 Ω in & out - $\beta = 10$ mc $f = 60$ m $G = 80$ dB




Unit #4 -

Oscillates under all conditions


Unit #1 - Received with open lead in B+ line
Oscillates with 0 bias - with ^{high} values of neg
bias and -2V and +110 on plates following
were taken


60 mc	-	$E_{in} - 90 \mu V$	$E_o - 1 V$	$\frac{I}{10^{-4}} = 10^4$
65	"	" 72	" 1V	
66	"	" 80	1V	
67	"	" 100	1V	
68	"	" 200	1V	
69	"	" 480	1V	
55	"	" 95	" 1V	
54	"	" 89	1V	
53	"	" 260	1V	
52	"	" 1000	1V	

Modified last stage of I as follows -

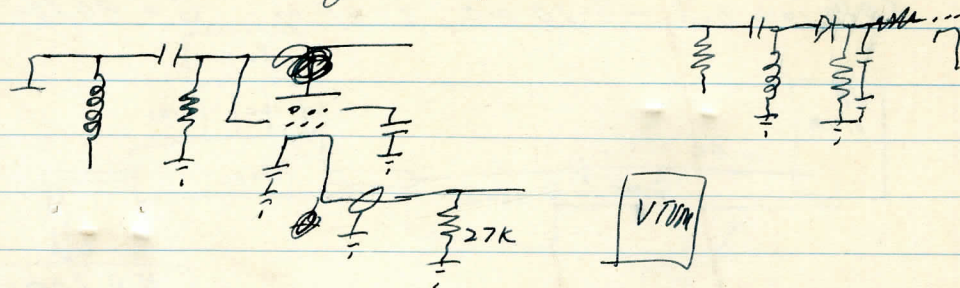

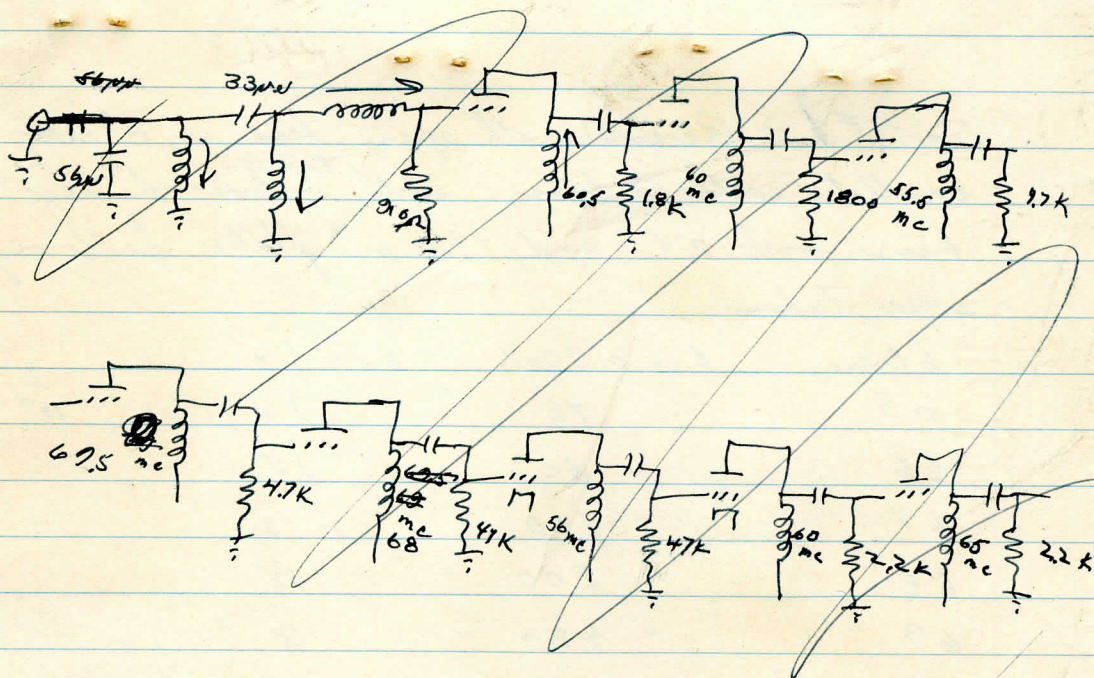Readings ~~was~~ indicated that gain was approximately same as before, however ~~dynamic respon~~ amplitude range was much greater



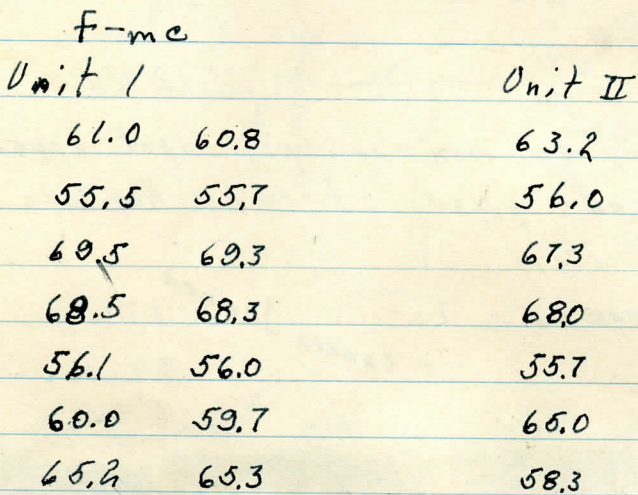

Handwritten circuit diagrams on lined paper:


- Diagram 1 (left): A series circuit with a battery, a switch, a resistor, and a light bulb.
- Diagram 2 (middle): A parallel circuit with a battery, a switch, and two parallel branches, each containing a resistor.
- Diagram 3 (right): A parallel circuit with a battery, a switch, and two parallel branches, each containing a resistor.

Nor21 - Test Exposure Necc. with 5XP-11 tube using Tetronix 217 scope
 Class L Film Exp. Date Dec 55 # 5232-383-1

		Sweep Speed	PRF	Acc	F
Roll 1	Run 1	250 mps/cm	1 KC	12 KV	1.5
	Run 2	200 mps/cm	1 KC	24 KV	1.5
	Run 1	"	"	"	1.5
Roll 2	Run	250 mps/cm	"	12 KV	1.5

Turned inten. up to max - i.e. until spot appeared
~~at left~~ placed pulse at 10 KC Rep Rate on trace
 & adj. to 1 cm

Roll 1	Run 1	250 mps/cm	1 K	Jammed 12 KV	1.5
	" 2	200 "	"	.. camera 24 "	1.5

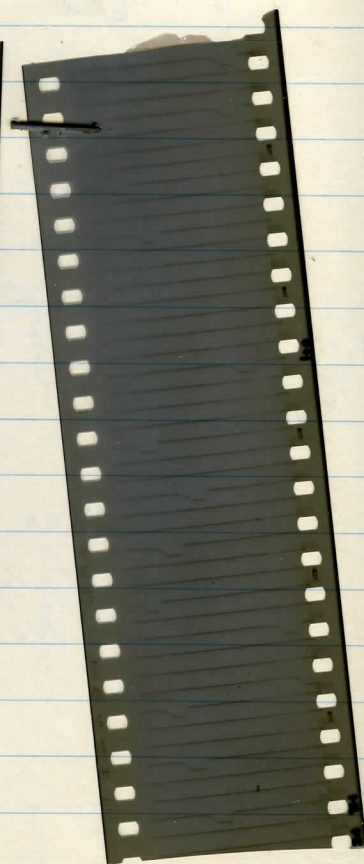




Run 1
 Roll #1

Run 2
 Roll #1

Run 1
 Roll #1


Run 1
 Roll #2

Nov 24

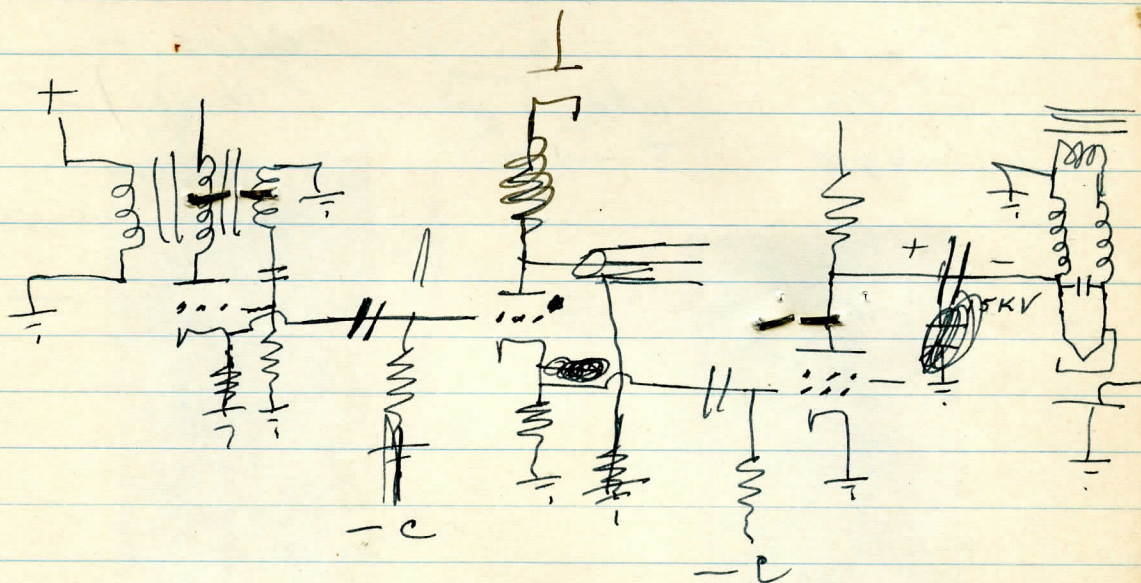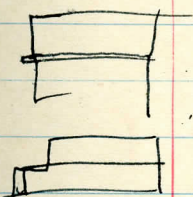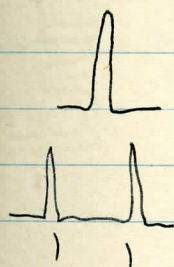


laid out above CKT with 2CR3 (Hg)
but deionization time defeated it.

Try the following-

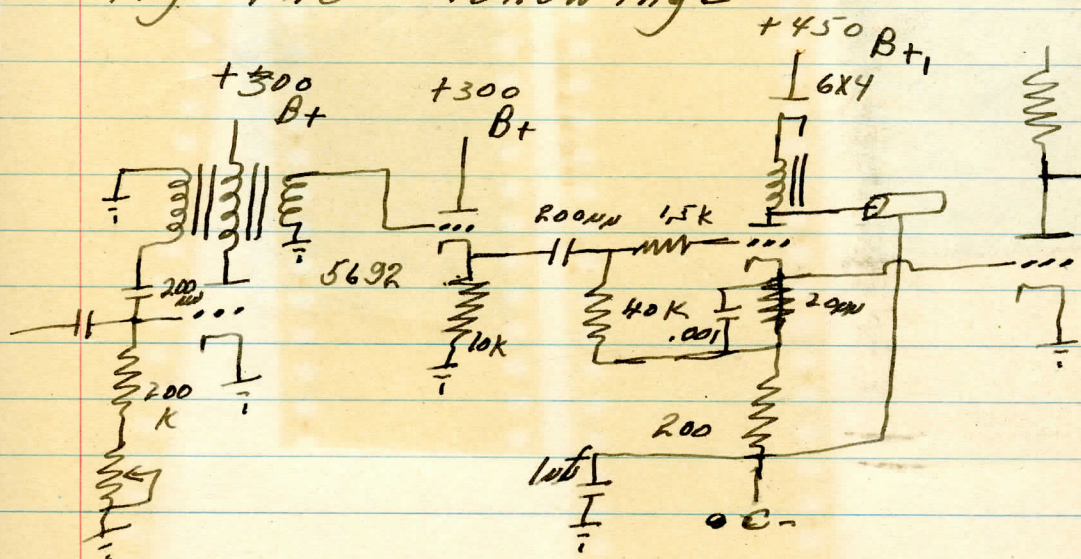

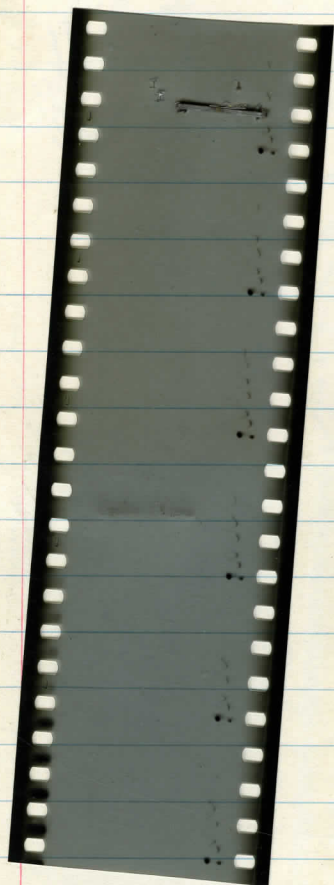
Mod II b FFI
Class K
F-16 on strike
Image



Mod II b FFI
Class L
F-16 on strike Image



Try this CKT-


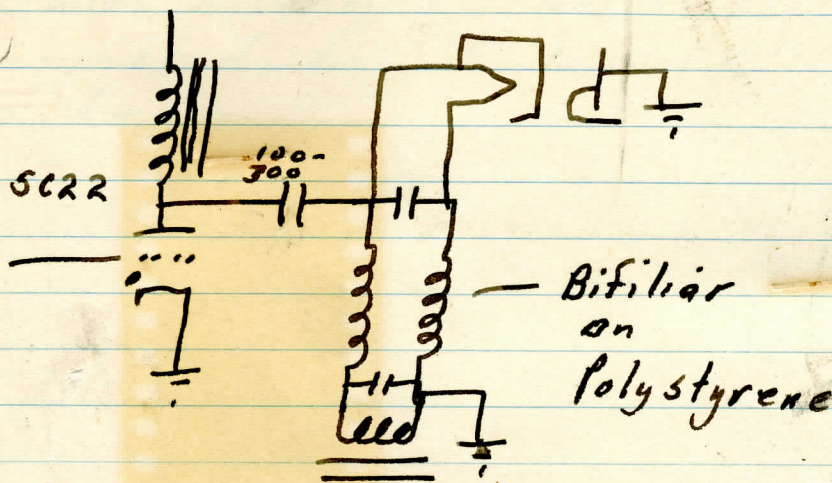


1/6/55 Build blocking osc which can be
synced to .8 to 1 kc - & to
2 mc -

M
N
O
P
Q
R
S
T
U
V
W
X
Y
Z

1/6/15

Test of distributed Amps-

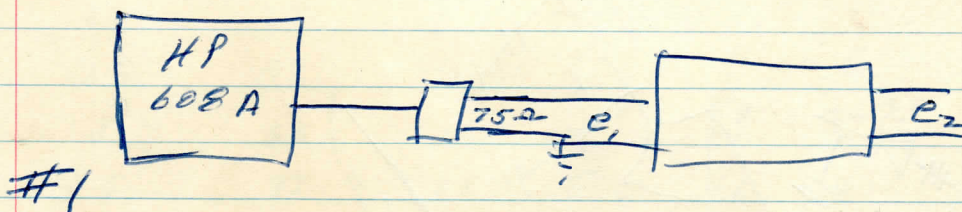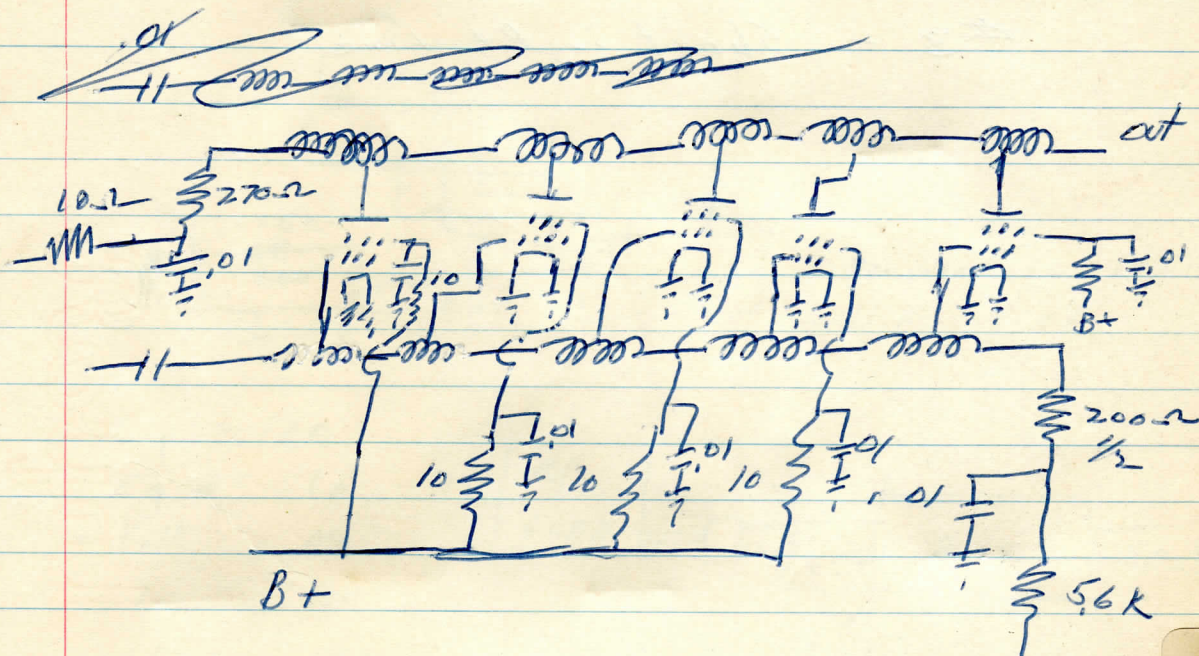


#1

@ - 2.35 V & B+118 $I_p = 82 \text{ ma}$
 $G = \frac{e_1}{e_2} = 7.3 \times 14$ @ 10.5mc

@ - 1.5V V B+118 $I_p = 130 \text{ ma}$
 $G = \frac{86}{5} = 17$ @ 10.5mc $\frac{5.6}{5} = 11$
 10mc @ $\frac{80}{5} = 16$ 75mc @ $\frac{78}{5} = 15$
 85mc @ $\frac{76}{5} = 15$ 95mc @ $\frac{65}{5} = 13$
 120mc @ $\frac{65}{5} = 15$ 130mc

#2 @ ^{2.8}~~-1.2V~~ B+12V
Gain looked OK @ 100mc


#3 - Short in B+ line

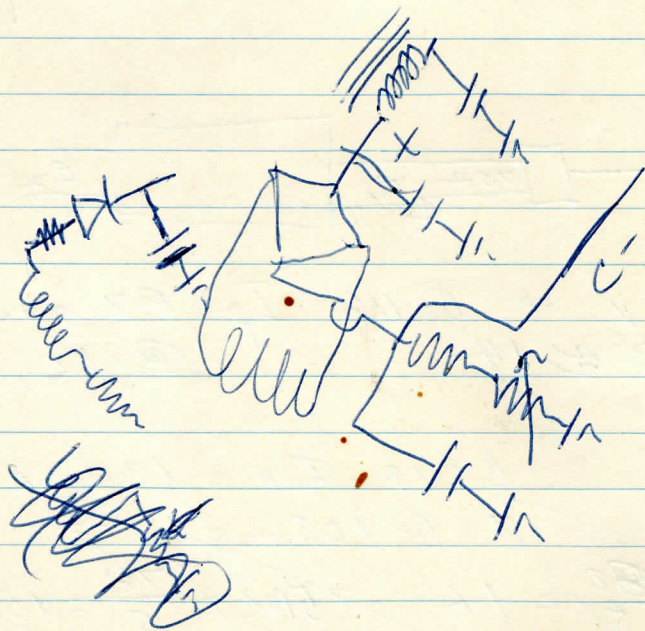

Run complete test on amps - unit #1
 Max on 6AK5 = 18 ma For strip of 12 tubes
 $12 \times 18 = 216 \text{ ma}$

18
 12
 36
 18
 216

900

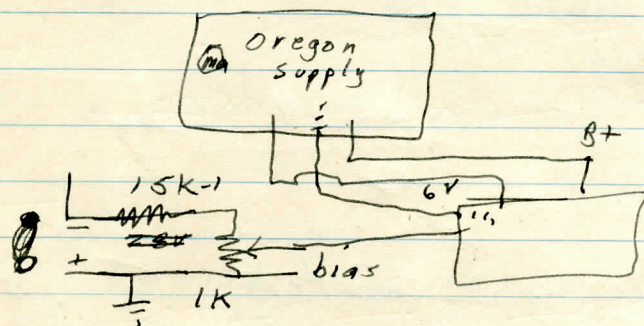

Measured V_s with
 HP 410A

$E_p = 120$
 $E_g \bullet I_p$
 - Volt Ma

H.P.
 60BA

Term
 inside
 cable

Amp

E_o

1 195
 1.5 159

2 121

2.5 92

3 65

3.5 47

4.0 30

4.5 20

$E_g = 1.5/K$

E_p

90 -76

100 95

105 105

110 112

115 122

120 132

F	E_{in}	E_o	G
m c	V	V	
10	.5	4.7	10.4
25	.5	4.6	8.1
50	.5	4.1	8.02
75	.5	4.6	8.12
100	.5	3.8	7.6
125	.5	3.8	7.6
145	.5	3.4	6.8
137.5	.5	2.4	4.8
146	.5	2.5	5
150	.5	2.5	5
155	.5	2.6	5.02
160	.5	2.5	

K
 $E_g = 1.5$
 $E_p = 120$
 $I_p = 130$

M
 O
 P
 Q
 R
 S
 T
 U
 V
 W
 X
 Y
 Z

Unit #1

f	e_{in}	e_o	G
mc	$\frac{1}{2}$	$\frac{1}{2}$	$\frac{1}{2}$
165	.5	3	6
170	.5	3.6	7.2
175	.5	4	
180	.5		
190	.5		
200	.5		

measuring devices off

Fry scale on meter

Using scale on meter

Sig Gen + VTVM are inconsistent
above 130 mc & below 20 mc

These measurements made using att on

Gen is std - measurements are obviously

subj. to error

$e_g = K @ .5V$
 f_{mc}

e_o	G
30 4.3	8.6
50 4.0	9
95 4.4	8.8 8.4
100 4.3 3.9	8.6 7.8
110 4.4 3.7	8.8 7.4
125 4.4	8.8 7.5
136 3.4	6.8
145 3.2	6.4
155 2.5	5.

Gain as f(ep)

Gain as $\frac{e_o}{E_{in} f}$ G Ep

f = 50 mc

90	5.6
100	6.8
110	7.8
120	8.8 9.2
130	10.4

$e_g = -1.5$ $e_p = 130$ $I_p = 180$

#2

$$E_p = 120 \quad I_p = 155 \quad e_g = -1.5$$

$$G = 8 \quad @ \quad 200mc$$

$$\#3 \quad E_p = 120 \quad I_p = 158 \quad e_g = -1.5 \quad G = 9 @ 100mc$$

$$\#4 \quad E_p = 120 \quad I_p = 150 \quad e_g = -1.5 \quad G = 8.7$$

$$\#5 \quad E_p = 120 \quad I_p = 180 \quad e_g = -1.5 \quad G = 9 @ 100mc$$

$$\#6 \quad E_p = 120 \quad I_p = 180 \quad e_g = -1.5 \quad G = 9 @ 100mc$$

$$\begin{array}{r} 270 \\ \times 0.02 \\ \hline 5.40 \end{array}$$

$$\begin{array}{r} .14 \\ \times .02 \\ \hline .0028 \\ \times .02 \\ \hline .0056 \\ \times .02 \\ \hline .0112 \\ \times .02 \\ \hline .0224 \\ \times .02 \\ \hline .0448 \\ \times .02 \\ \hline .0896 \\ \times .02 \\ \hline .1792 \\ \times .02 \\ \hline .3584 \\ \times .02 \\ \hline .7168 \\ \times .02 \\ \hline 1.4336 \end{array}$$



$$P = 12A$$

39

$$\begin{array}{r} 15 \\ 12 \overline{) 18} \\ \underline{12} \\ 60 \end{array}$$

180

O
P
Q
R
S
T
U
V
W
X
Y
Z

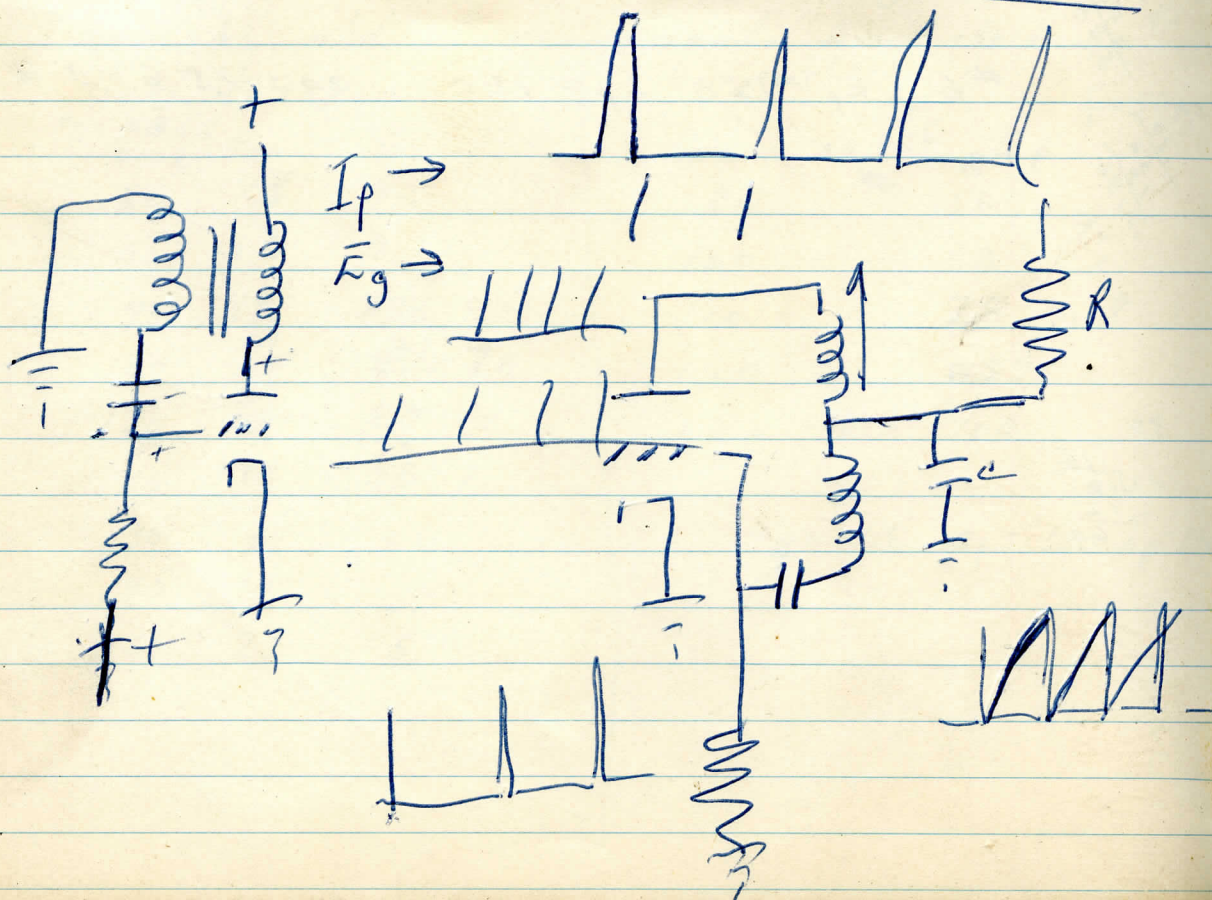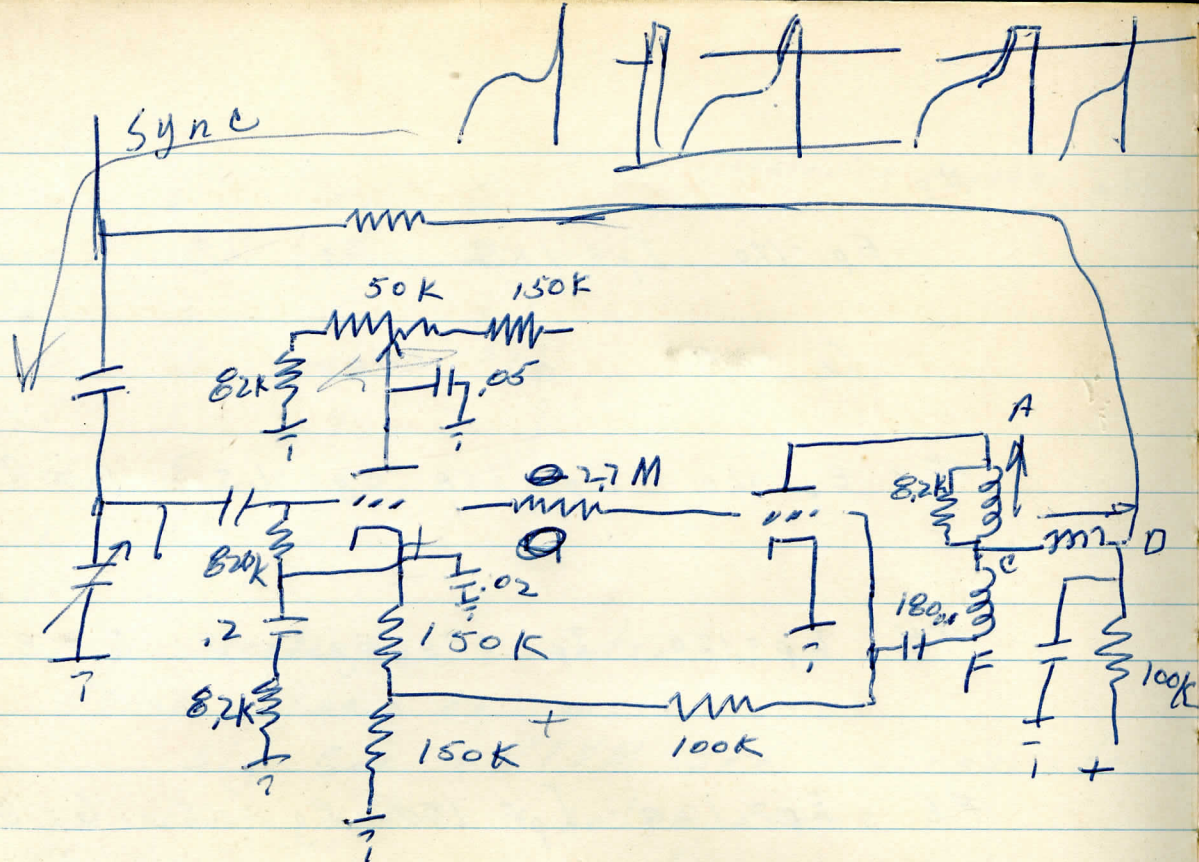


Set up M & b as test Veh. for M3



change sweep length to max of 35-40ns
and add gain control to V amp.

Add Range MKs if possible—



Modification

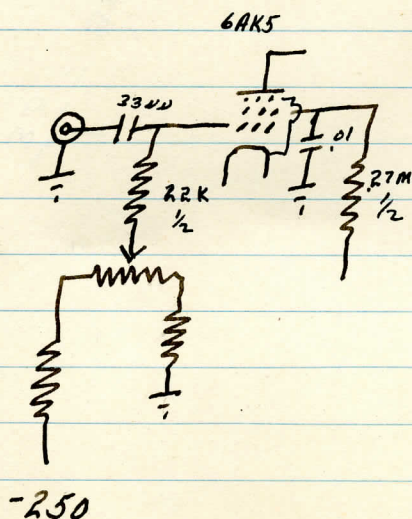

$$X_c = \frac{1}{2\pi f C}$$

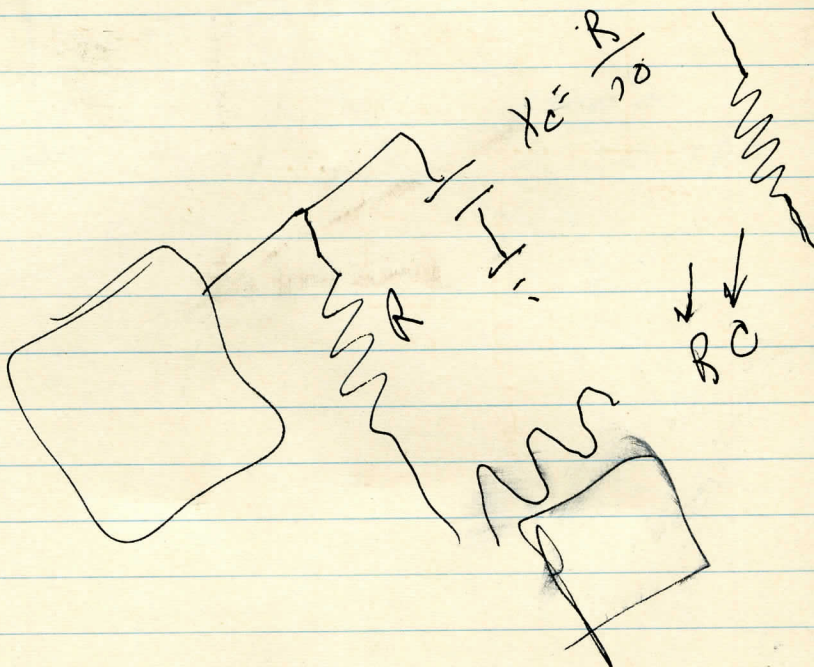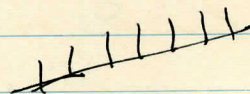

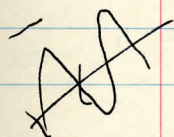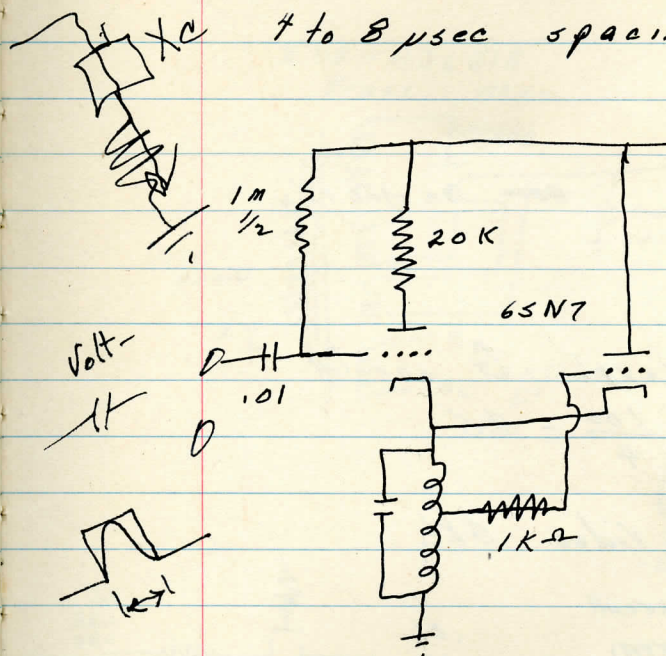Pulsed L/C oscillator to generate
time fiducial for M3
4 to 8 μ sec spacing



$$X_c = \frac{1}{2\pi \cdot 10^5 \cdot 0.1 \times 10^{-6}}$$

$$= 6.3 \times 10^1$$


$$= 66 \Omega$$

$$1000 \Omega$$

P
Q
R
S
T
U
V
W
X
Y
Z

Video Amp. for M-3
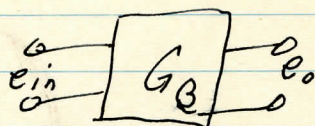
$$\tau = \frac{1}{2} \times 10^{-6} \text{ sec } C_0$$



3JP. C.R. tube defl. ~~80~~ 90-120V/in


e_{in} - noise is 4V

assume same signal level G should

$$\frac{100}{4} = 25$$

$$\frac{4 \times 10^4}{2.5 \times 10^4} =$$

Use standard 6AG7 4mc Video Gkt.

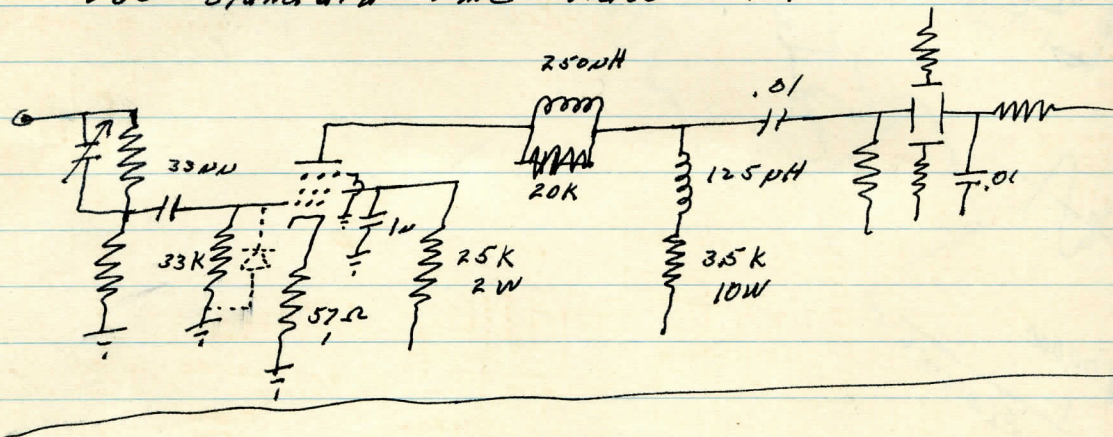

$$2.2 \times 1.5 \times 10^3 \times 4.5 \times 10^{-12}$$

$$2.2 \times 10$$

$$5 \times 10^{-8}$$


$$\frac{1}{A} = \frac{1}{A_1} + \frac{1}{A_2}$$

$$\frac{1}{A} = \frac{1}{100} + \frac{1}{150}$$


$$\frac{1}{A} = \frac{3}{300} + \frac{2}{300}$$

$$\frac{1}{A} = \frac{5}{300}$$

Power Supply for M1a + M3 A scopes

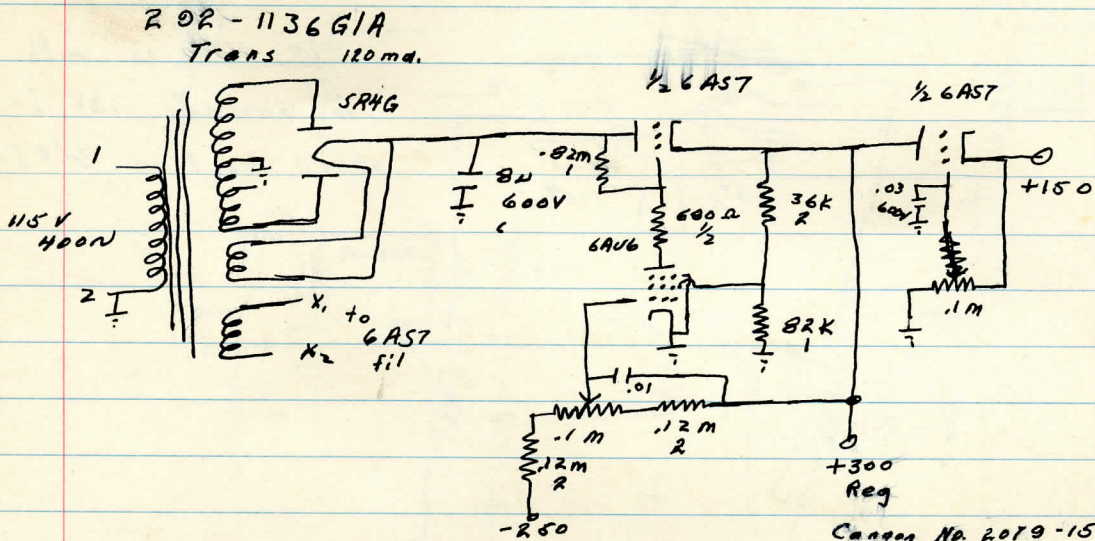


Cannon No. 2079-15

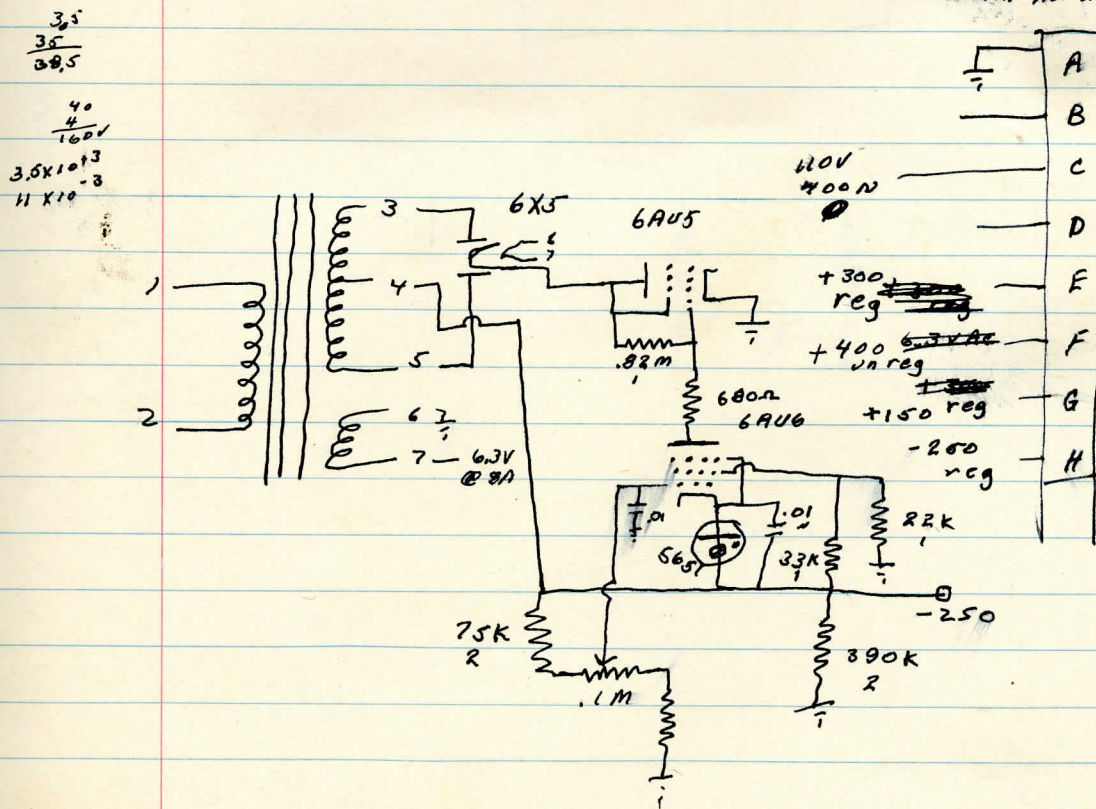


Q
R
S
T
U
V
W
X
Y
Z



Differential Relay

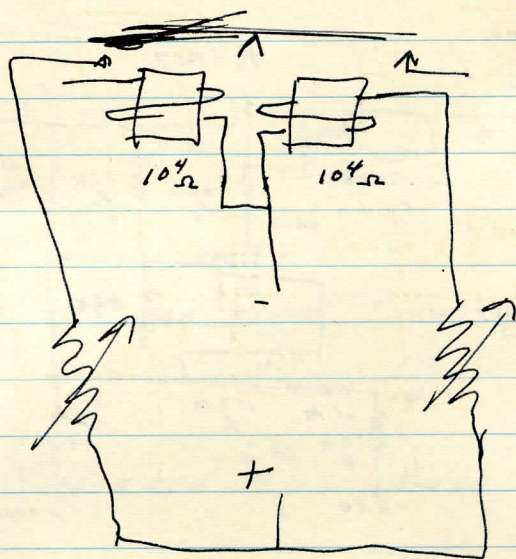

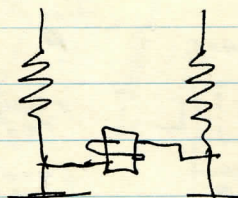
to pull in with
 in one coil $13V$ $I = \frac{13}{10^4} \times 1.3mA$
 other must be $4.4V$ $I = 4.4mA$



Pulse ckt. for osc. time fiduc.

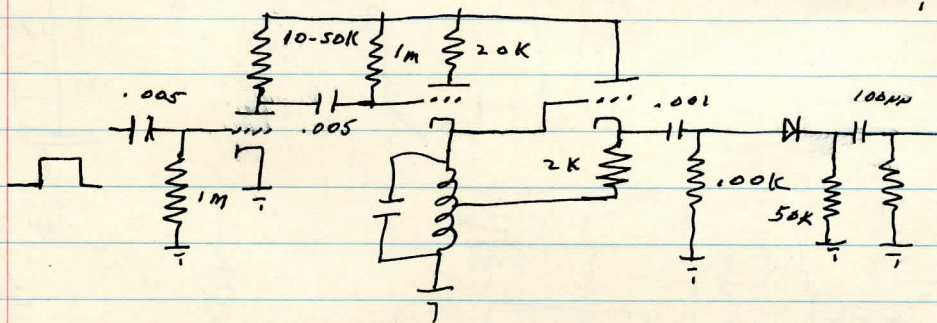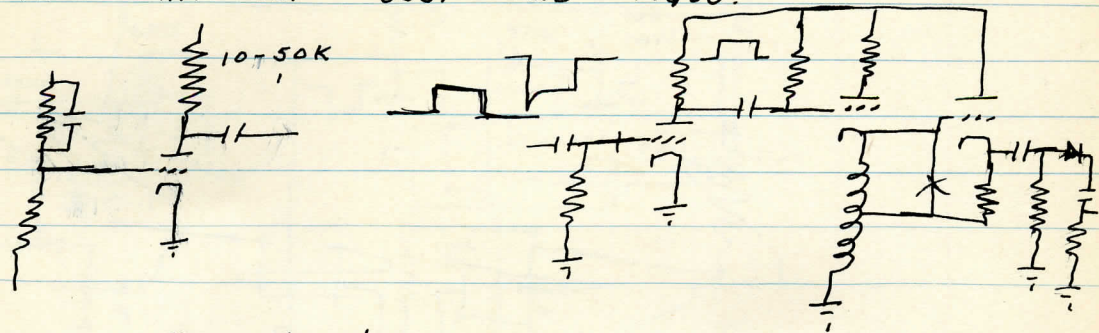

Q
R
S
T
U
V
W
X
Y
Z

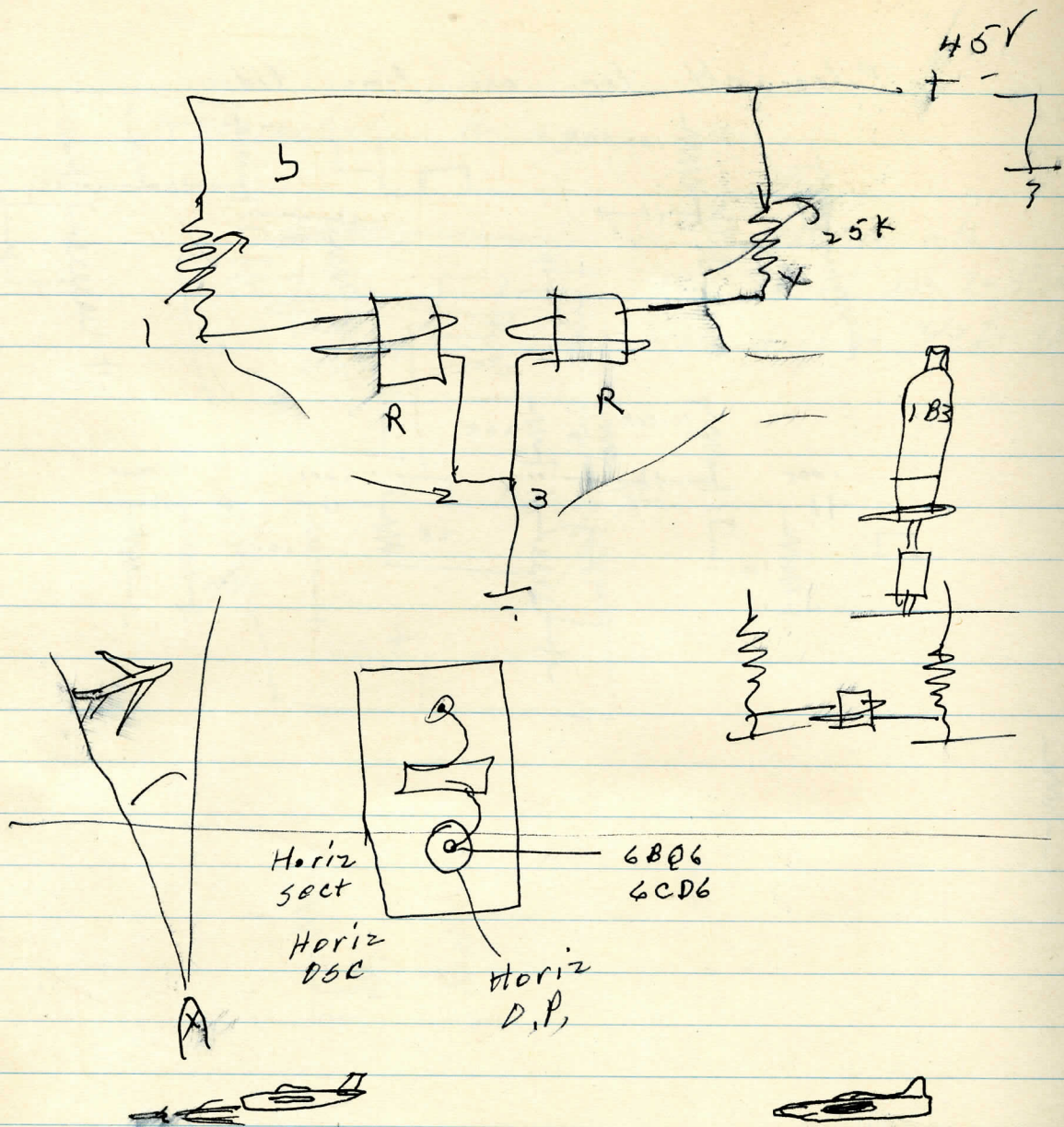

$$I = \frac{E^2}{R}$$


$$\sqrt{R} = F \quad 2.5 \times 10^4 \quad 5 \times 10^2$$

Holcher


~~40~~ MIV

Ascope ± G-40

1.3 mi r

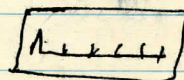

A 6

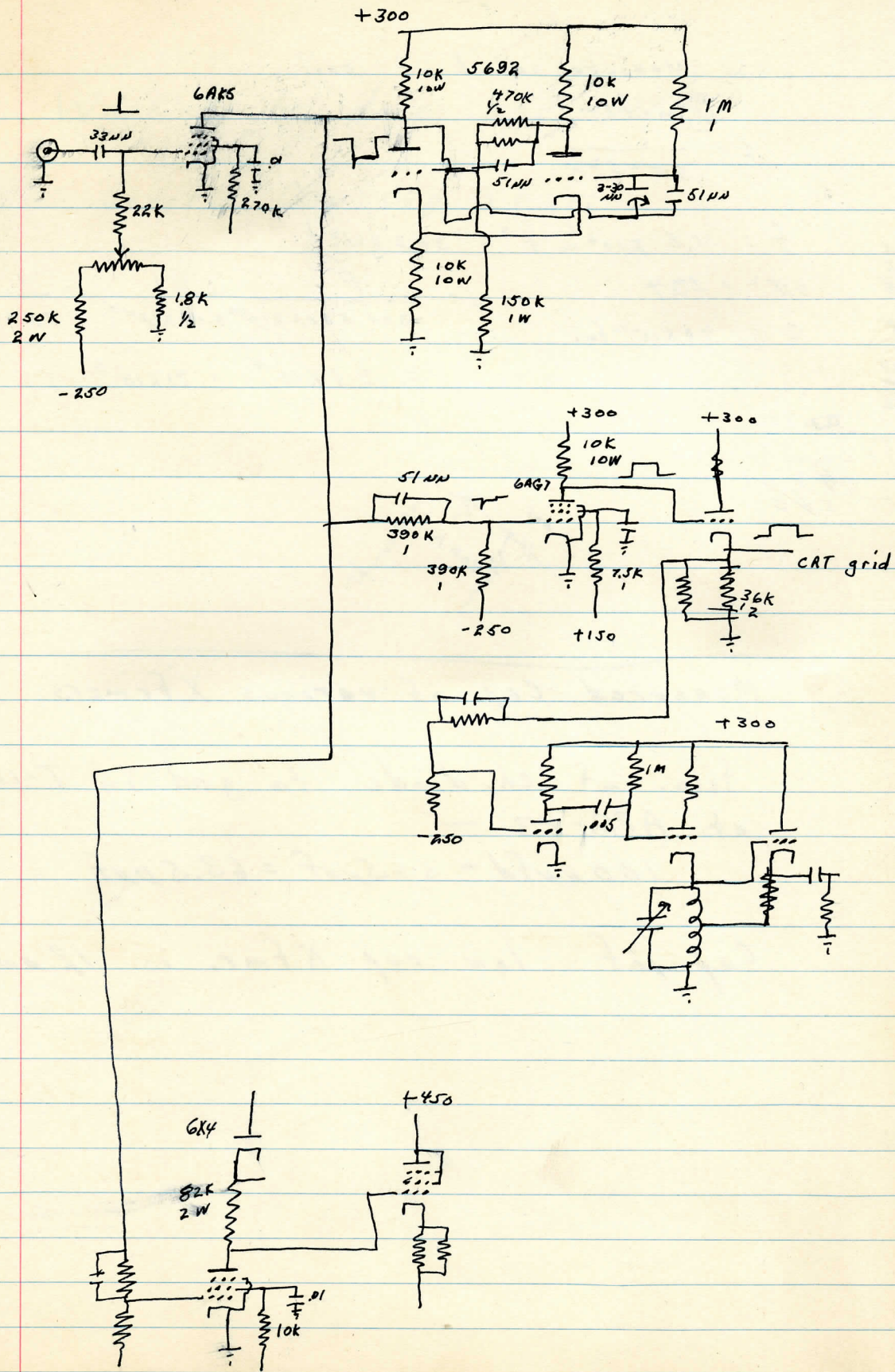

$$\frac{.02}{6800 \sqrt{150,000}}$$

 E

R
 S
 T
 U
 V
 W
 X
 Y
 Z

Measure induct of coil

Q meter

$$L = \frac{1}{4\pi^2 f^2 C}$$


$$f = 5.5 \times 10^6 \sim f^2 = 30.2 \times 10^{12}$$

$$4\pi^2 = 39.4$$

$$C = 40 \times 10^{-12} \text{ far.}$$

$$L = \frac{1}{39.4 \times 30.2 \times 10^{12} \times 40 \times 10^{-12}} = \frac{1}{39.4 \times 30.2 \times 4 \times 10^4} = .21 \times 10^{-4} = 21 \times 10^{-6}$$
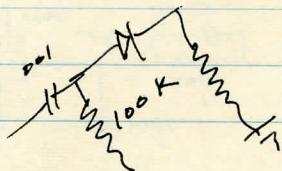
$$\begin{array}{r} 58 \\ 55 \\ \hline 275 \\ 275 \\ \hline 30.25 \\ \hline 394 \\ 31 \\ \hline 1182 \\ .4 \\ \hline 4.72 \end{array} \begin{array}{r} 21 \\ 0.21 \\ 1.000 \\ 954 \\ \hline 560 \end{array}$$



Measured Cap of various Xfmr's.

fil's. of ch. diode to gnd in T-1201
of APS-23 —





$$100 \mu\text{fd} - 36.5 \mu\text{fd} = 63.5 \mu\text{fd}$$

Cap of low cap Xfmr. is 12 μfd

Work to be done on M-4

Const. low Cap. & Fmr.

R
S
T
U
V
W
X
Y
Z

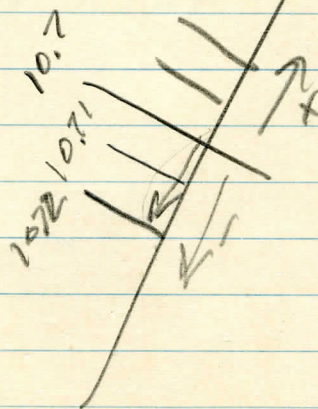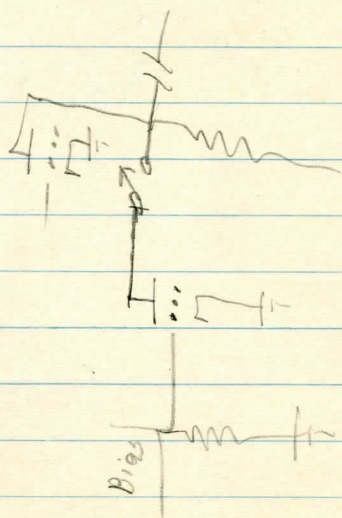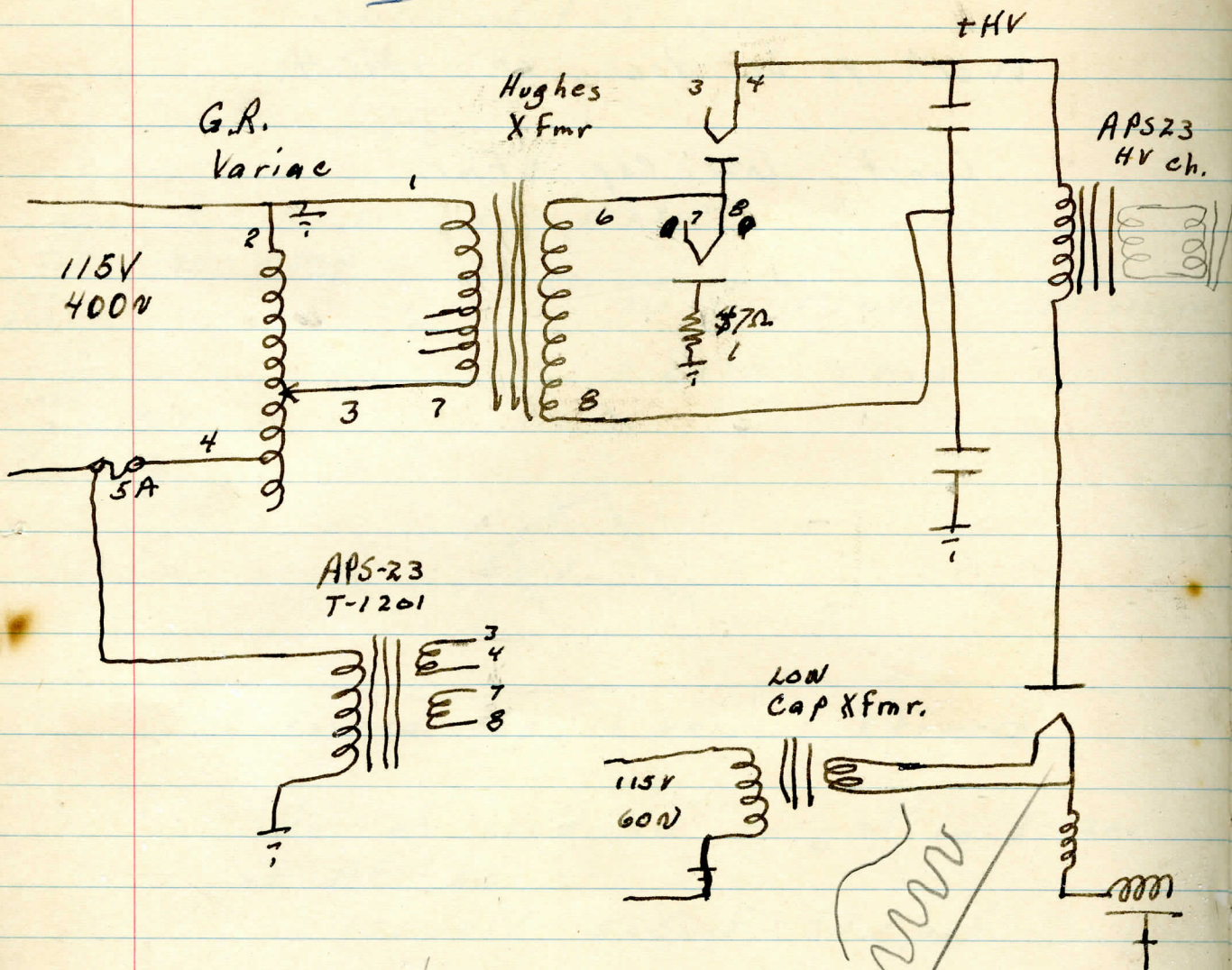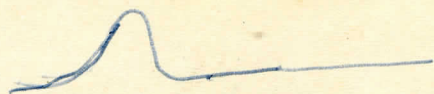

M-3 set up — 1/26/55

3.5
5
+75

5 μ sec sweep —

adj all Volts — 250 + 300 + 150

10 use

Film assessment

12

A Run 1 — B.S. — 3 mi — 8.5 div —

3.5
60

2 — B.S. — 2 mi — 6 div

36
420

3 — B.S. — 1 " — 3 div

4 — shot at 1 mi. rocket faintly visible

5 — " " 2 " " undet

6 — " " 3 " " "




Work to be done on A scope
For Fri's mission.

Change Hi Volt XFmr.

Lower Amplification

Add — B.O. time Fiduc —

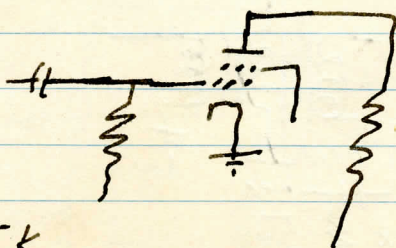

3.5k

S
T
V
V
W
X
Y
Z

Det need for peaking —

Decrease Amp by $\sqrt{3}$ — $\frac{3500}{3} = 1160 \text{ Hz/2000}$

$$R_T = 2.2 \text{ R.C.}$$


$$R = 1.2 \times 10^2 \text{ } C = ?$$

$$R.T. = 2.5 \times 10^{-6}$$


$$.25 \times 10^{-6} \text{ sec} = 2.2 \times 1.2 \times 10^3 \text{ } C$$

$$C = \frac{.25 \times 10^{-6}}{2.6 \times 10^3} \approx 1 \times 10^{-8} = \frac{1000 \times 10^{-12}}{.1 \times 10^{-8} \times 10^3} = .1 \times 10^{-9} \approx 100 \times 10^{-6} \times 10^{-3} \approx 100 \times 10^{-12} = .1 \times 10^{-5} =$$


OK

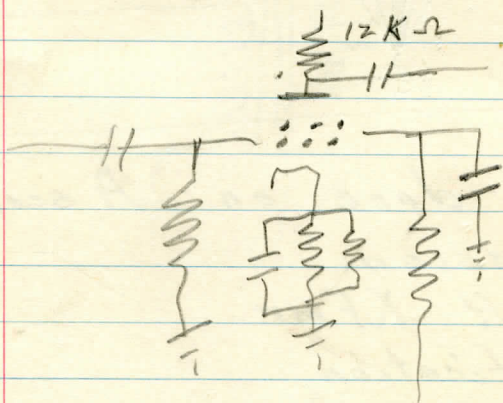


B.O.

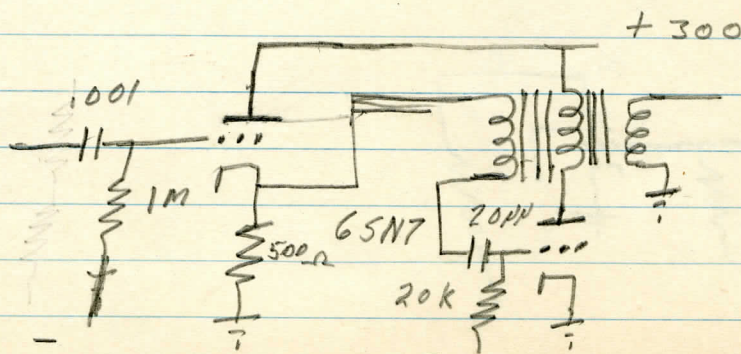

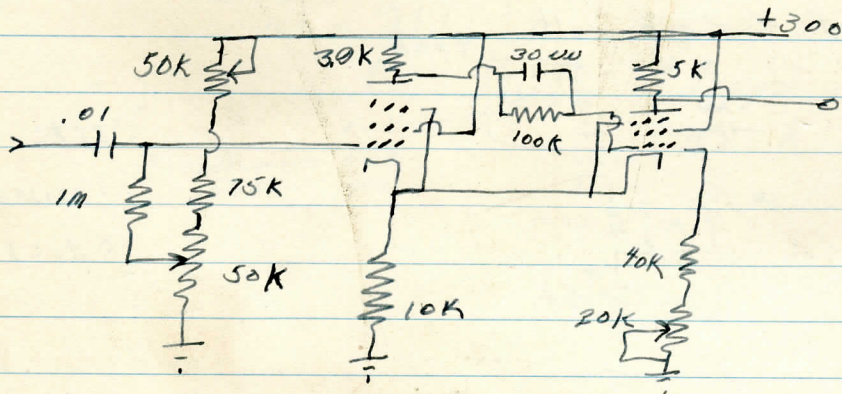Examine limiting properties of the ckt -
Try this discriminator




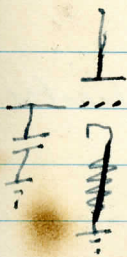
$$\frac{9 \times 10^4}{150 \times 10^4}$$



Circuit is tricky - has neg-undershoot - unstable
will not accept pulses less than 10 V Amp -
tends to go into a relatively long quasi-stable
state

1hr to try these ckt's

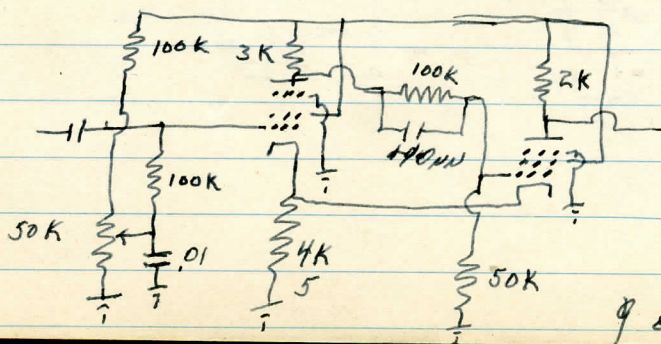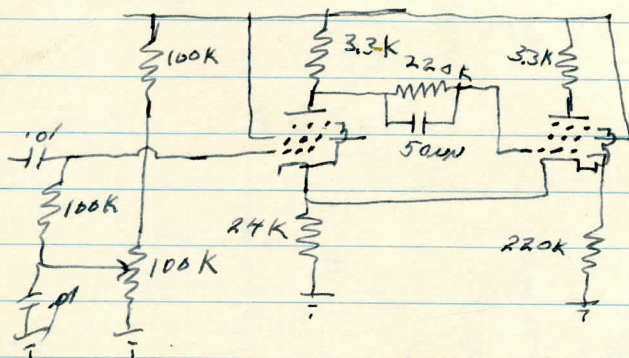

Displayed
about the
same character-
istics of the
other
go to sat-Amps

S
T
V
V
W
X
Y
Z


9 $5 \times 10^{-3} \times 5 \times$

$g_m \Gamma_p = .005 \times \frac{500}{2.500}$

6 AK5 - grid or plate sat -

Input - 2-8 volts

+120

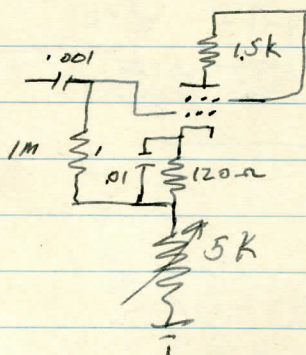

$$\begin{array}{r} 15 \\ 3.3 \\ \hline 2.5 \\ 16.5 \\ \hline 66 \\ 82.5 \end{array}$$

2.2 RC

$$= 2.2 \times 10^{-3} \times 2.5 \times 10^{-11}$$

$$= 8.25 \times 10^{-8} = .08 \mu\text{sec}$$


Looks good - With low plate Voltages it easily saturates
Gain works ok.

at 30V ~~2.5~~ B+ limits to 10V out at +4V in


120 @ 10 mA .01 30,000

$E = 1A$ $\frac{30}{.01} = 3$



$\frac{2 \times 10^4}{3 \times 10^4}$

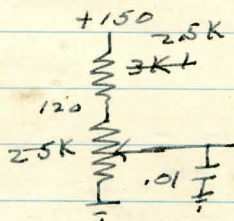

Try this

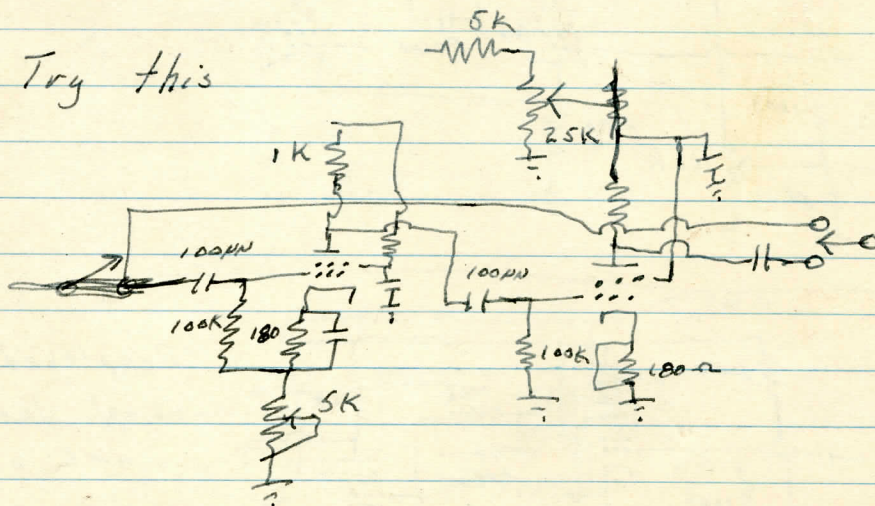


Tried 6AK5 for relay tube to use in

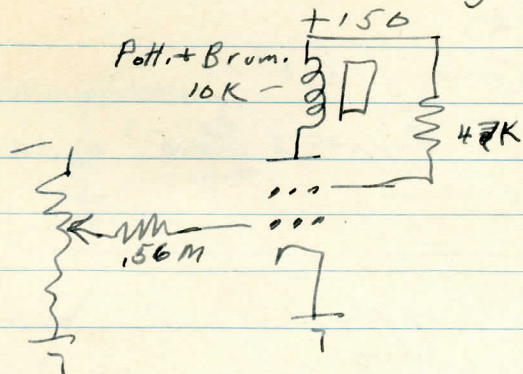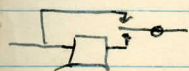


pulls in at -3.9
 ~~-2.5~~ V
 drops out at -2.6 V
 Look O.K.

Try Pulsed Blocking Osc —

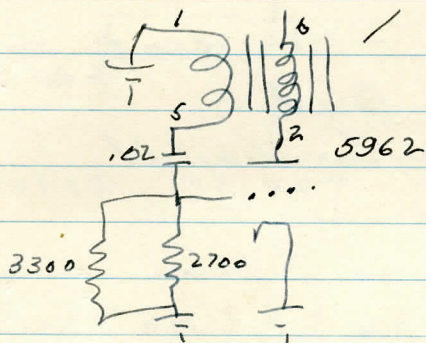With C-81 osc x fmr
 pulses could be obtained
 as fast as $-.25 \mu\text{sec}$



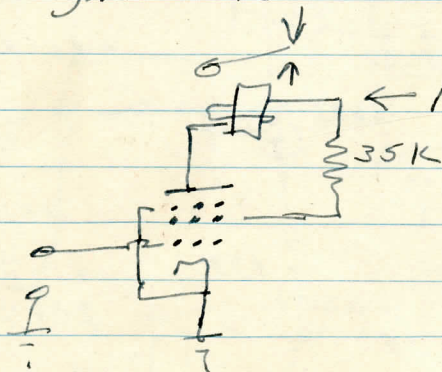F system AGC bias is approx -1.5 for
 no signal to -8 for signal



← 10K P+B relay
 adj. to pull in
 at -3.5 out at -4.5

$$\frac{0.10 \times 10^{-3}}{.98 \times 10^{+9}} = 10 \times 10^{-6}$$

$$10^{+9} \times .1 \times 10^{-3} = .1 \times 10^6$$

2/5/55 Test H.V. Supply

Hookup according to Tek-517 ckt & using their transformers

Some discrepancies in the measured values of + & - H.V. - - H.V. seems high may be caused by no load -

10KV adjustment seems limited

- 250 -

10 KV

20 KV

No load on HV

- 225 -

22 ma


22 ma

+ 400 -

30 ma


67 ma

Fix up P.E.C. ckt

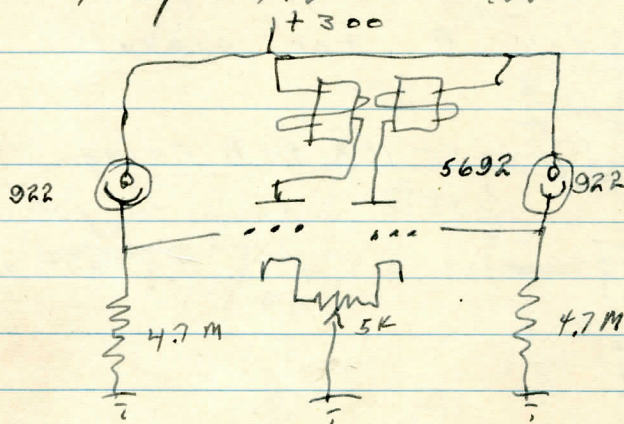


differential relay was extremely insensitive


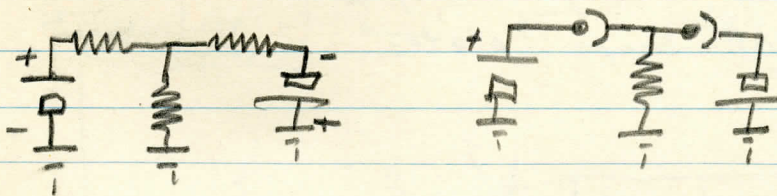
$$\begin{array}{r} .4V \\ 20ma \quad 4 \overline{) 2000} \\ \underline{.02} \\ 20 \overline{) .40} \end{array} \quad \begin{array}{r} 50 \\ 200 \overline{) .002} \\ \underline{.400} \end{array}$$



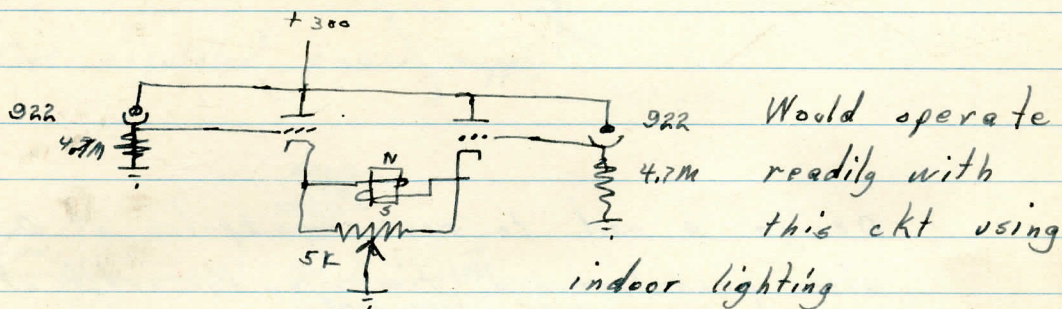Tried Barb. Col. 'Micro positioner', a polarized relay coil D.C. res of $\approx 200 \Omega$ would operate readily on .4 W which is current sens. of $\frac{.4}{200} = .002 A = 2ma$ -




Might try these -

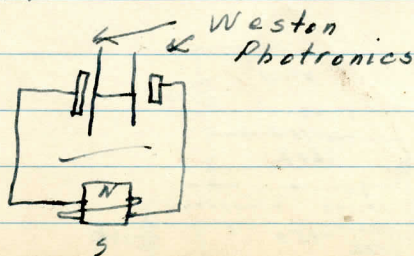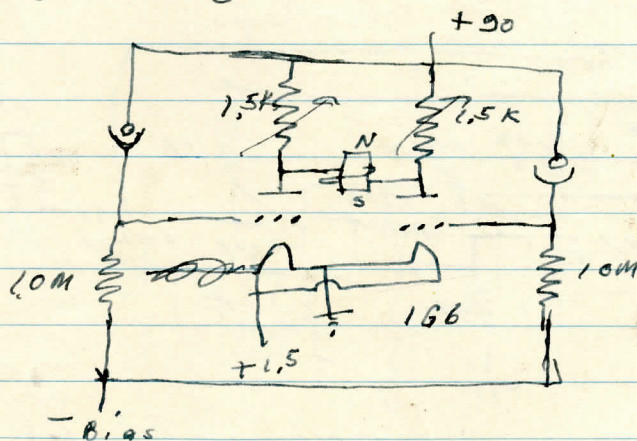


T
V
V
W
X
Y
Z

Design a Hi Voltage probe for direct coupling to 5XP-scope plates


100Vcm

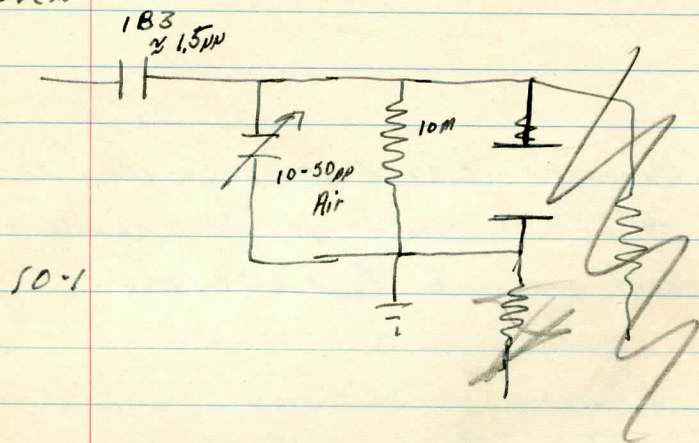

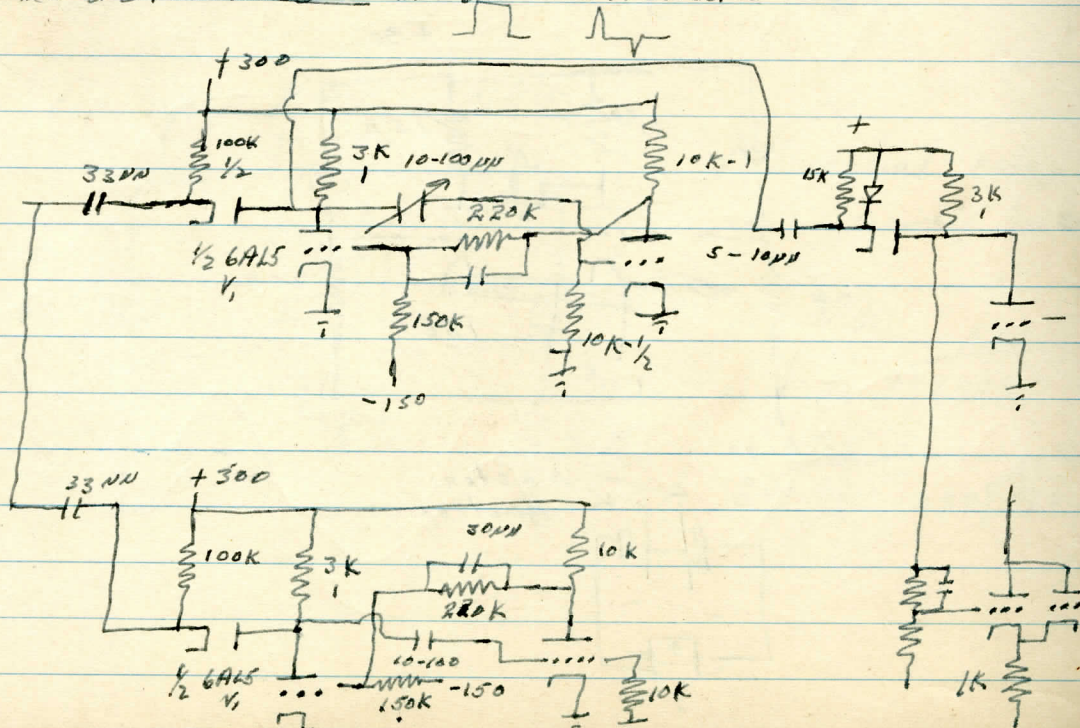Design a unit to receive a pulse at 0 time and after predetermined times on the order of 1 to 5 μsec generate two ^{time independent} pulses of ½ μsec whose phase ~~can be determined~~ ~~in~~ be controlled.



gm rp

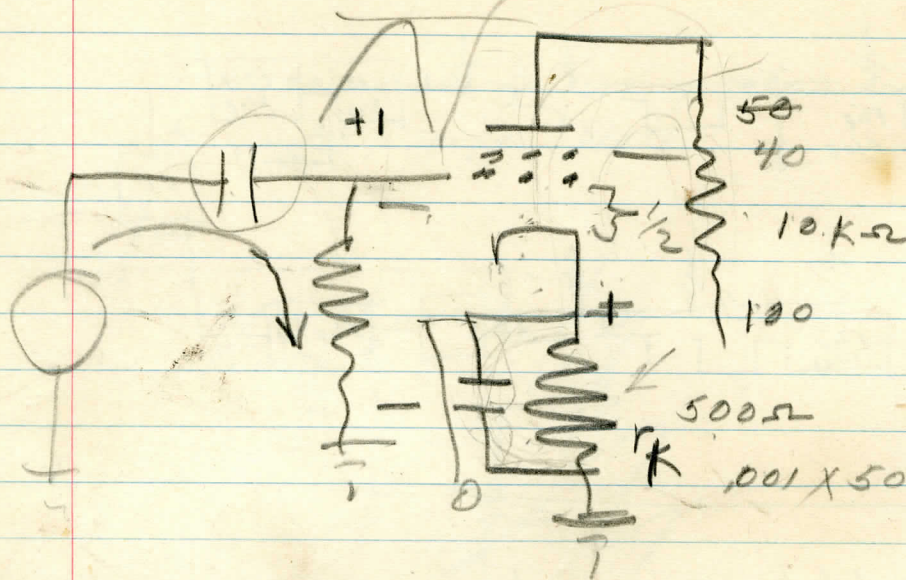

$10^4 \times 10^{-3}$

35

25

$$\frac{21}{90}$$

117
91 91 4

$$\begin{array}{r} 15 \overline{) 26.00} \\ \underline{15} \\ 11 \end{array}$$



200

$$.001 \times 500 = .5V$$

$$\begin{array}{r} 26 \\ 26 \\ \hline 156 \\ 52 \\ \hline 676 = 34 \\ \hline 200 \end{array}$$

$$X_c = \frac{1}{247 \text{ fC}}$$


$$X_c = \frac{R}{10}$$

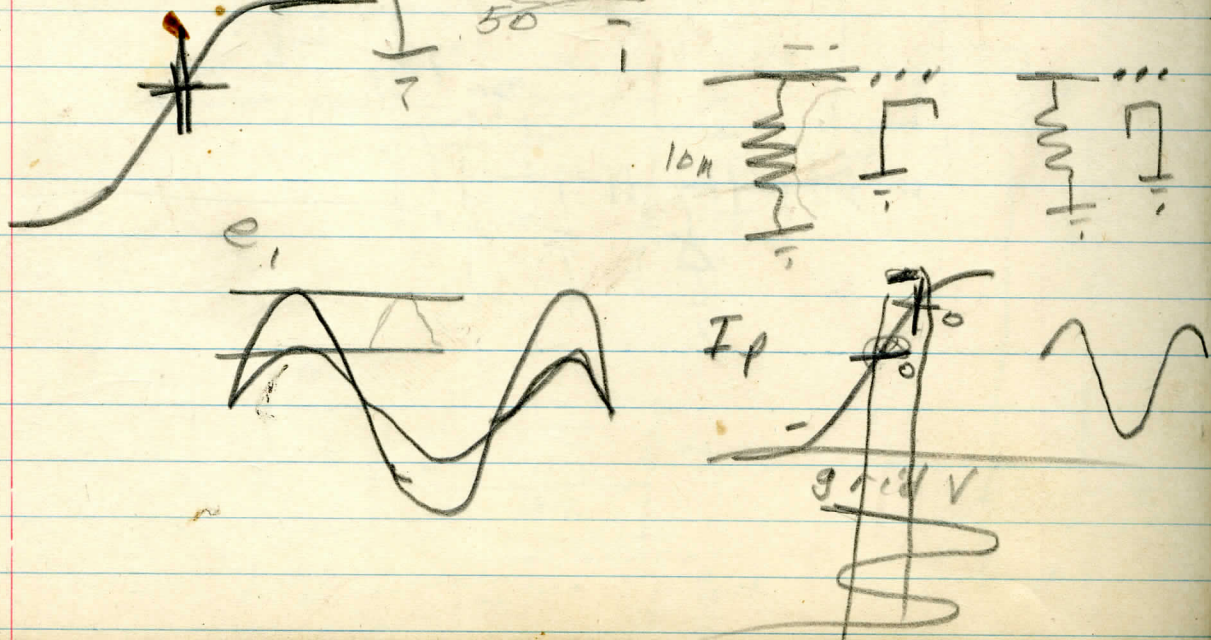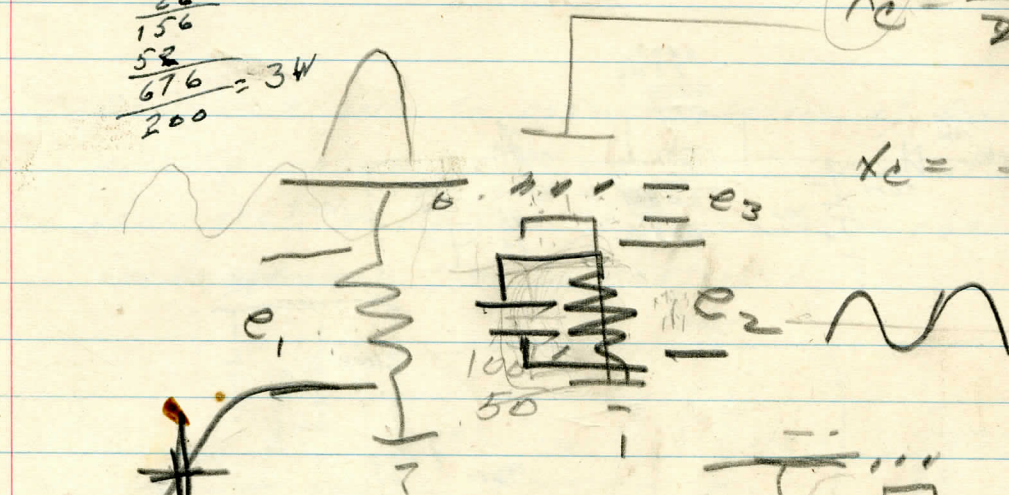

Check out Chain Video Amp


1-2-3

B1-W4-Red

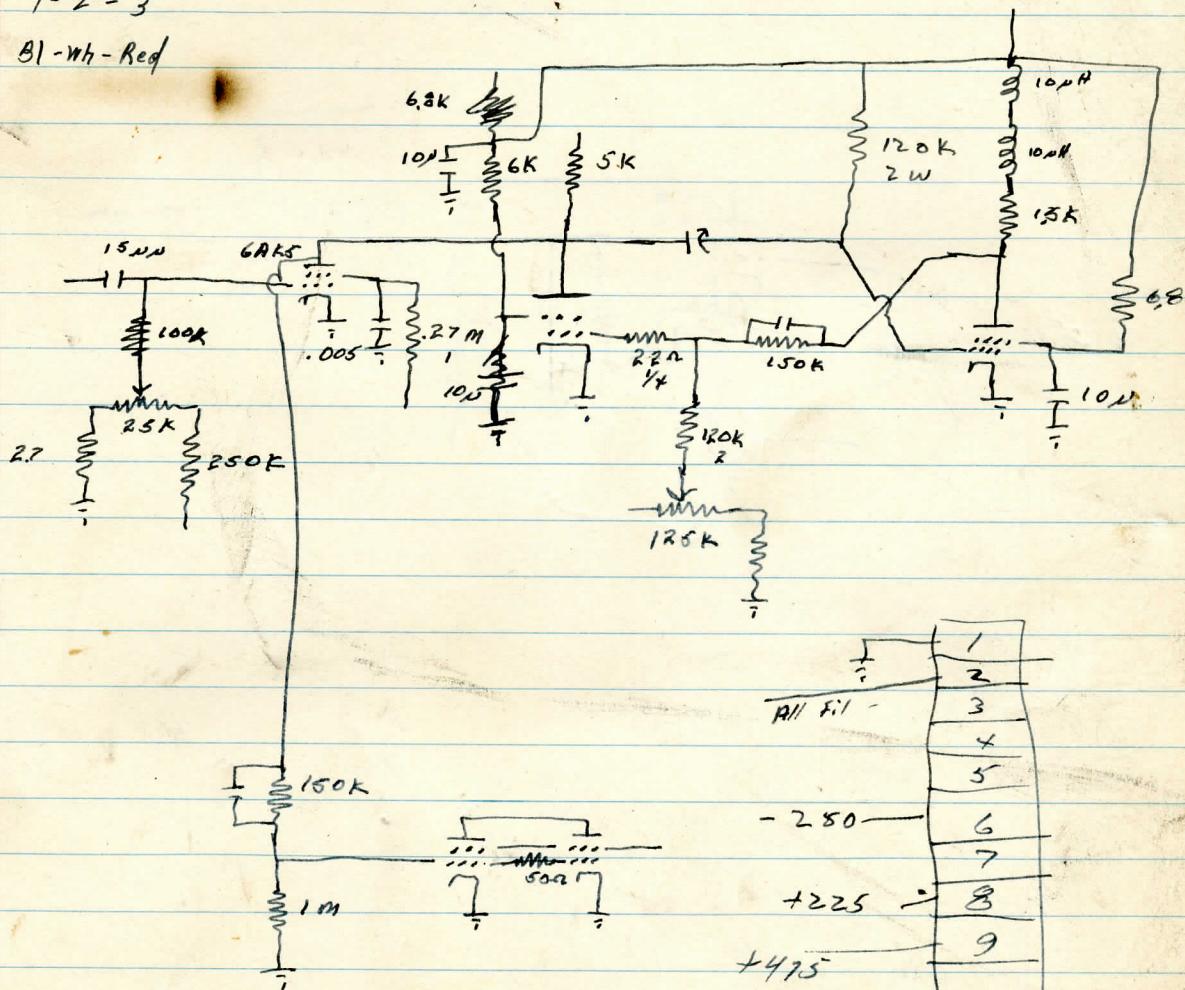

1	1
2	2
3	3
4	4
5	5
6	6
7	7
8	8
9	9

T
V
V
W
X
Y
Z

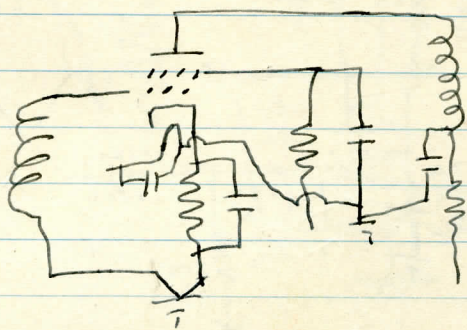


Test Video Amp -

3

~~Bore~~


Pre Amp
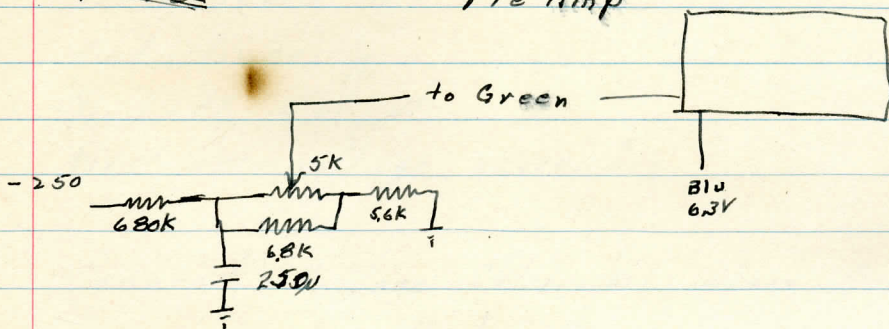
$$\begin{array}{r} .16 \\ 16 \\ \hline 96 \\ 16 \\ \hline 2.56 \end{array}$$




Bread board a ^{sweep} n.ckt. suitable for M-3
 Med linearity
 Hi Volt Output
 First det- Voltage necessary

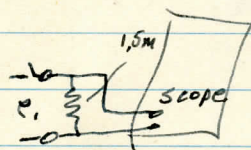Comared Voltage Calibrators whose Outputs were
 inconsistent - Used setup below to check calibrators




cal w ser # 977 was 54 V @ 50 V
 ser # 674 " 65 V @ 50 V

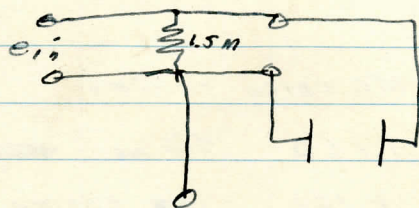Check defl factor of 5XP. CR tube
 on 10 KV pos 8.4 KV 19 KV installed in Tek 517
 20 " " 17 KV 3.9 KV



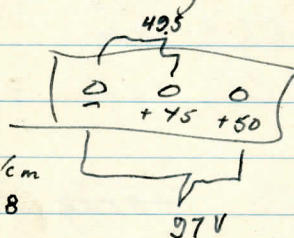Pin supplied from Dry
 Batter Rayovac #107R6055



10 KV pos	24 KV pos
49 V - 9.5 mm	49 V - 5 mm
51.5	98
97 V 19 mm	97 V 9.5 mm
51.0	102
100 39 mm	390 V 3.75 "
48.7	104
151.2	1304



AV 50.4 V/cm or Vin AV 101. V/cm =

Tube face = 11.8 cm

10 KV ace = 595 V 24 KV = 1090 V

~~Shoot for Voltage of 800~~ try -250 +300 +150 +
Stick with Tex 517-




V₀

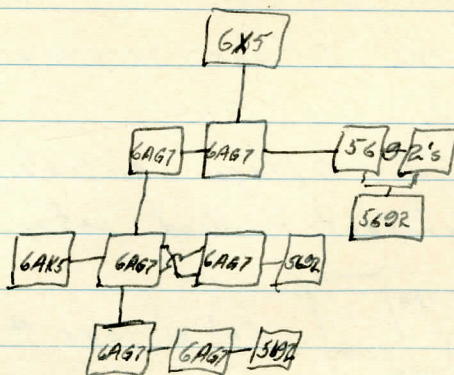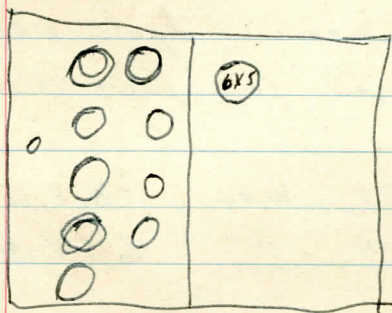


~~Layout~~ Sweep Ckt
Pwr Supplies

Power for sweep


-250	reg	- 50ma	+ 350	unreg	- 100ma	
+225	reg	- 450 ma	+150	470 ma	100ma	10mV ripple
+475	reg	- 150 ma	+180	250ma	unreg	
+ 250	^{reg} unreg	50ma				

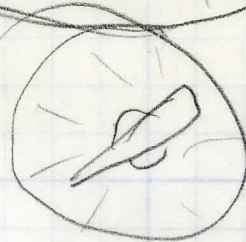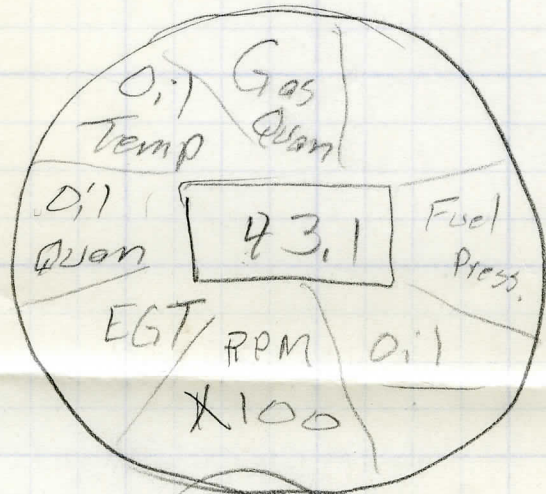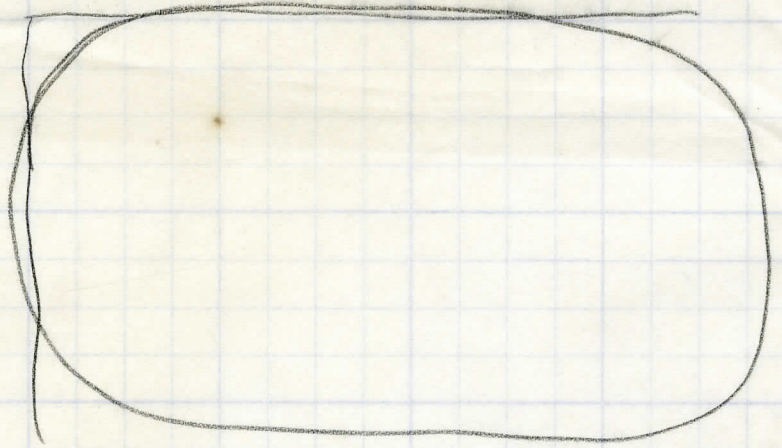


checked Hughes Xfmr 420-70-0891

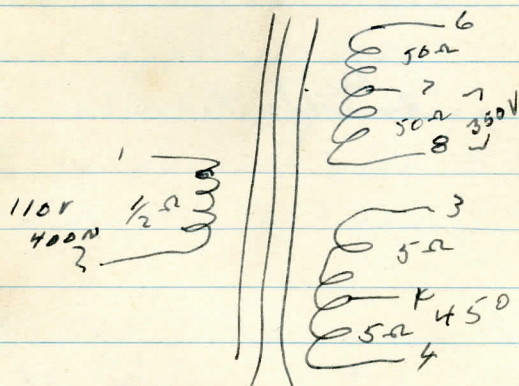

Peerless 42070-082T

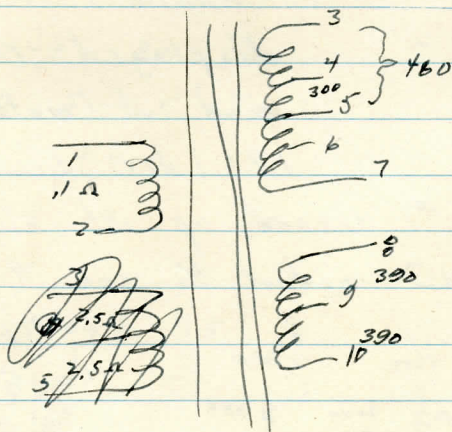

Peerless

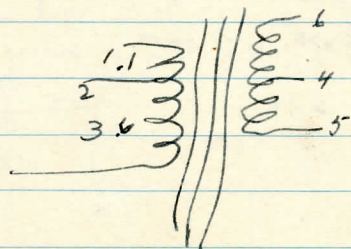


V
W
X
Y
Z

Checkout CKts on audio osc & Master Trigger

Audio Osc using Am. ^{Time} Std. Fork

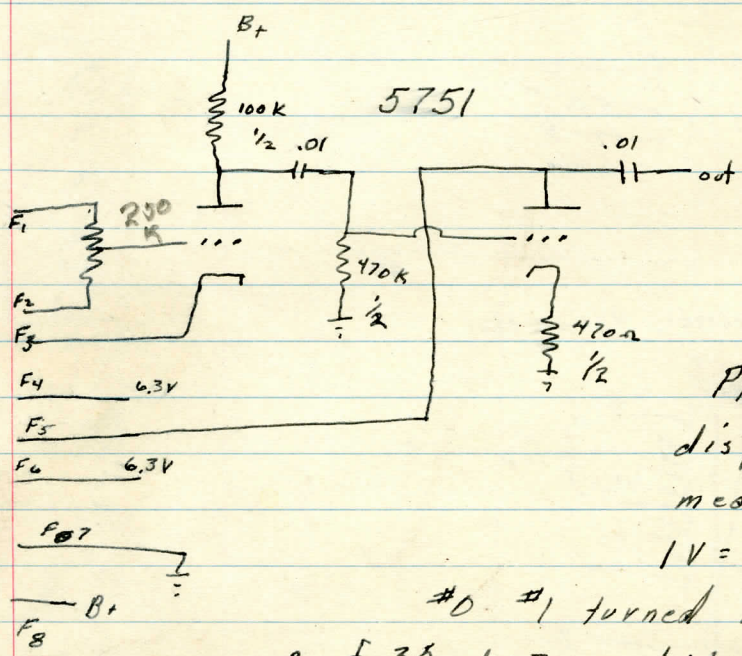$\frac{2.5}{30}$
 $\frac{5}{6} \times \frac{68}{5} = 58$
 $\frac{6}{340}$
 $\frac{30}{30}$



Wave form - dist
Sine wave
Vout 16 div


Photo 1 3 cycles
displayed - reticle Full up
med int (matched reticle)

1V = 1 div directly into scope

#0 #1 turned up int slightly f. 3.5

2 - f 3.5 med.int. 3 - med.int. 1/2 sec 4 - 1.5 sec med.int.

5-

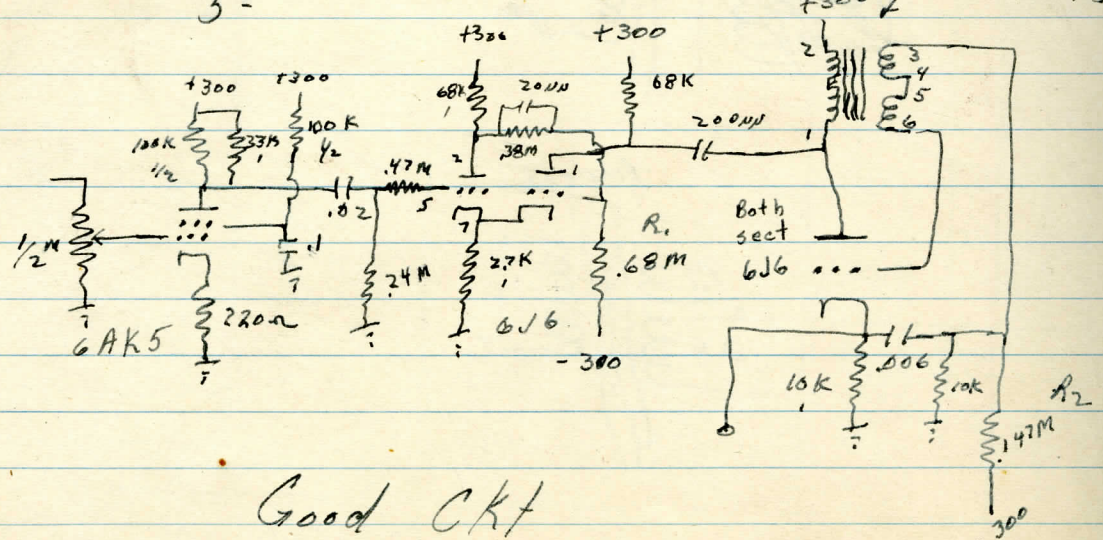


Good CKT

Current @ 300 V For pulser & time std. ~ 20ma

The preceding ckt gives pos pulses of $\approx 200V$ A which apparently have little jitter - Test further for effect of phasing & environmental effects to compensate for $-250V$ bias drop r_1, r_2 to $500K$ & $120K$ resp.




- square wave
1 div = 50V
3 cy
- #5 Ret full up - F-3.5 $\frac{1}{30}$ sec 3 cy From Pin 2
of multi 1 div = 50V
 - #6 f- 5.6 $\frac{1}{30}$ med int
 - #7 F-3.5 $\frac{1}{2}$ sec med int
 - #8 " " 1.5 " " "
- sq w.
1 div = 50V
Pin 1 multi
3 cy
at pl. of
Amp
1 div = 50V
Plate of
B.O. 1 div = 2V
- #9 F-3.5 $\frac{1}{2}$ sec " "
 - #10 F-3.5 $\frac{1}{30}$ " "
 - #11 F-3.5 $\frac{1}{30}$ " "
 - #12 " " $\frac{1}{2}$ " "
 - #13 " " $\frac{1}{2}$ " "
 - #14 " " $\frac{1}{30}$ " "
 - #15 F-3.5 $\frac{1}{30}$ med int pulse out Tek. Scope 12KV
 - #16 F-3.5 $\frac{1}{30}$ " " pulse out 1 cm = 2.5 usec

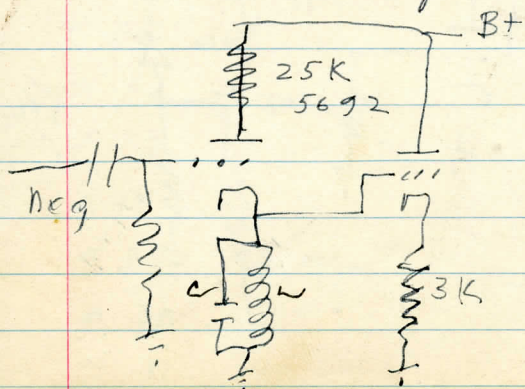Try a ringing ckt for possible use with J Scope




By using ckt below with various values of c & L sine waves with ~~various~~ almost negligible ~~values~~ damping -

W
X
Y
Z

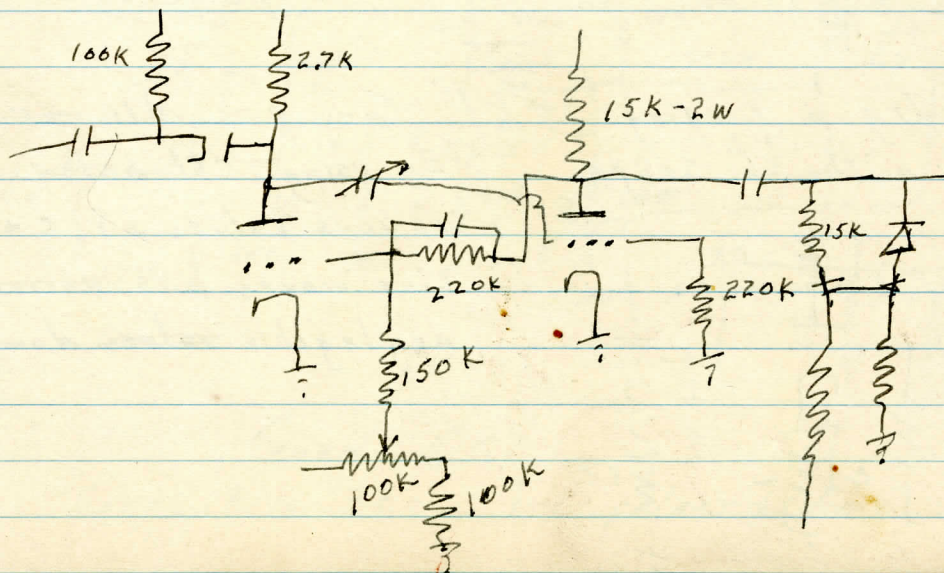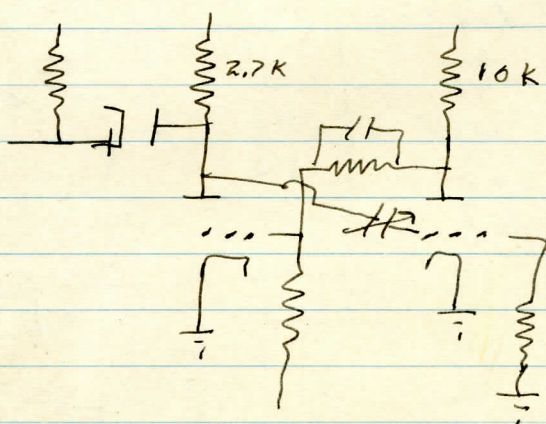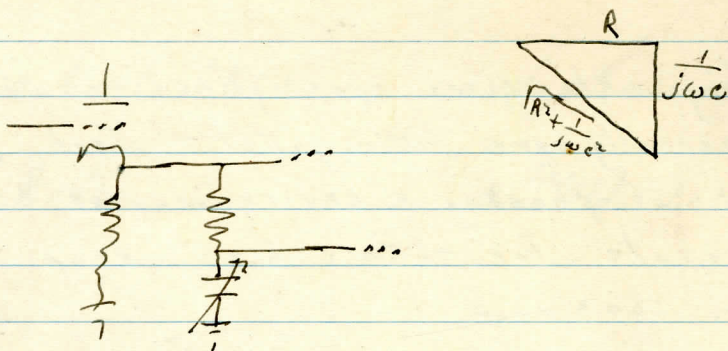

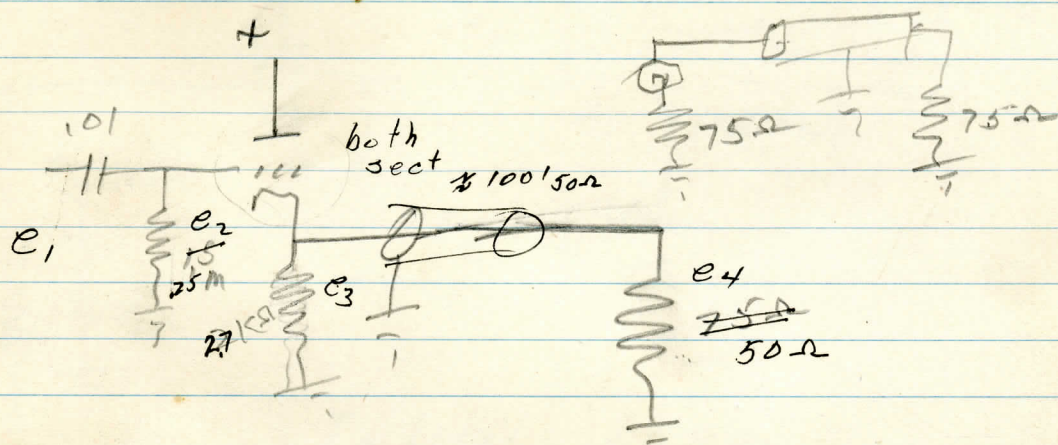2/23/55 Cathode Follower to transmit $\frac{1}{2}$ usec signals @ 25'




Tried	5844 -	6J6	G
I_p	15ma	10ma	2.5
E_b	105V	105V	2.5

Photo #18	XX	F 3.5 $\frac{1}{3}$	60 cps	24KV	2.20 cm	9.8 v/cm
#19	"	"	"	"	"	"
#20	"	"	"	"	"	"
#21	"	"	"	"	"	"
#22	"	"	"	"	"	1.8 v/cm
#23	"	"	"	"	"	"
#24	"	"	"	"	"	"
#25	"	"	"	"	"	"
#26	"	"	"	"	"	"
#27	"	"	"	"	"	"
#28	"	"	"	"	"	"
#29	"	"	"	"	"	"
#30	"	"	"	"	"	"
#31	"	"	"	"	"	"

Poss double

2/24/55

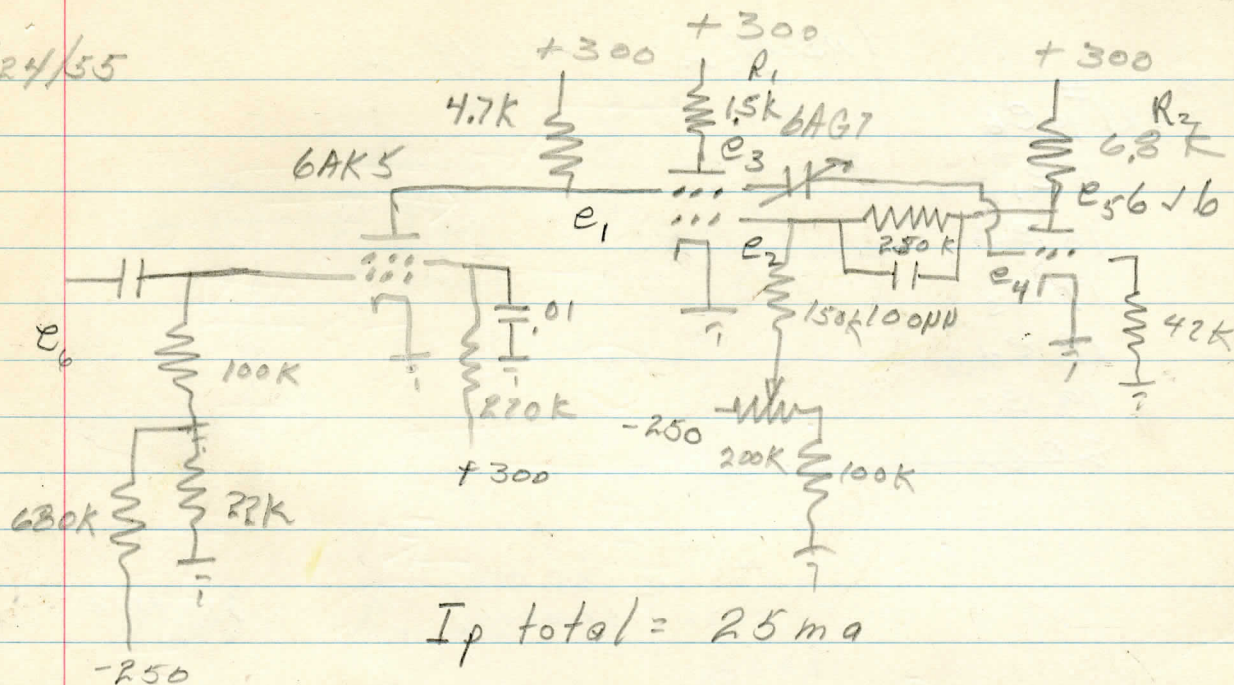

Tried this ckt - Output Amplitude was insufficient even with larger Values of R_1 - e_5 sloped badly

Photo ~~2~~


F-3.5 - $\frac{1}{30} \times \times$

PREF=60	#1	12KV	e_6	$\frac{1}{2} \mu \text{sec}$	cm	46 V/cm
	#2	"	e_1	1 μsec	"	"
	#3	"	"	"	"	"
	#4	"	e_2	"	"	"
	#5	"	e_2	"	"	"
	#6	"	"	"	"	"
	#7	24KV	e_6	2 μsec	cm	"
	#8	"	e_6	$\frac{1}{2} \mu \text{sec}$	"	"
	#9	"	e_1	"	"	"
	#10	"	e_3	"	"	"
	#11	"	"	"	"	"
	#12	"	e_3	"	"	"

X
Y
Z

1 nsec/cm 46 V/cm

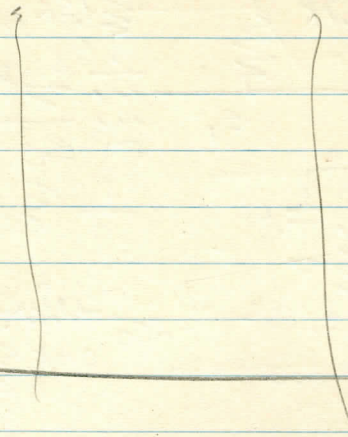60 n
24 kV #
14 e6
15 e1
16 e2
17 e3
18 e4
19 e5
20 e6




$$10^3 \times 9 \times 10^{-8}$$

$$\begin{array}{r} 60,000 \\ .0025 \overline{) 150.0000} \\ \underline{150} \end{array}$$

$$10^3 \times 15 \times 10^{-12} = 15 \times 10^{-9}$$

$$= 0.15 \times 10^{-4}$$

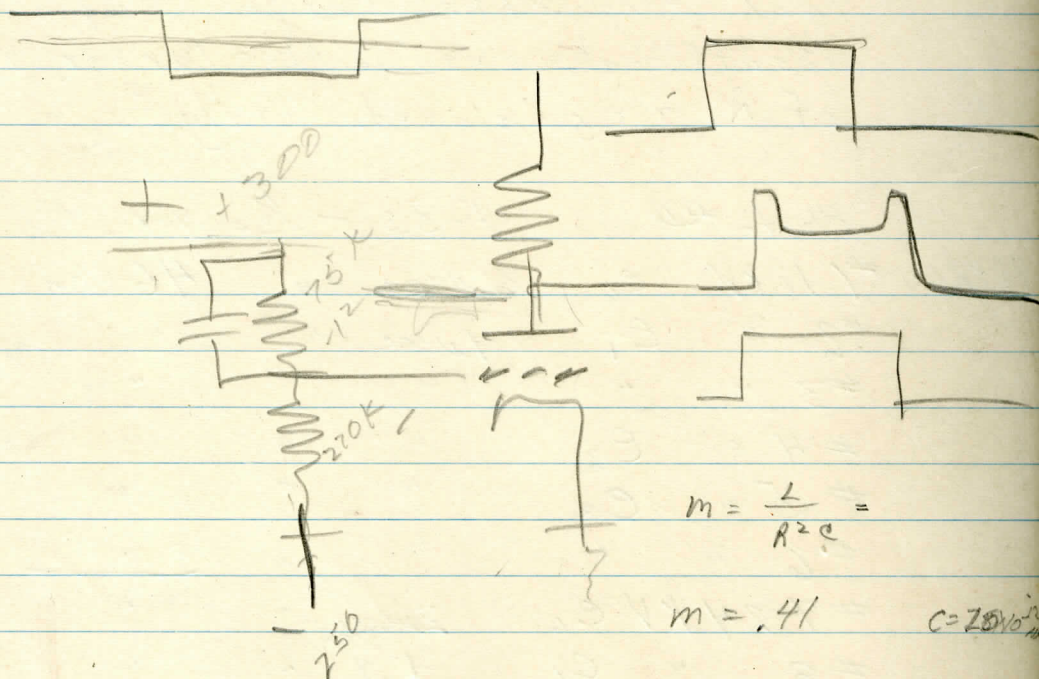


$$m = \frac{L}{R^2 C} =$$

$$m = .41$$

$$C = 20 \times 10^{-12}$$

$$\begin{array}{r} .12 \\ .82 \overline{) 1.00} \\ \underline{.82} \end{array} \quad .41 = \frac{L}{10^6 \times 20 \times 10^{-12}}$$

$$L = \frac{1}{.82 \times 10^{-6}}$$

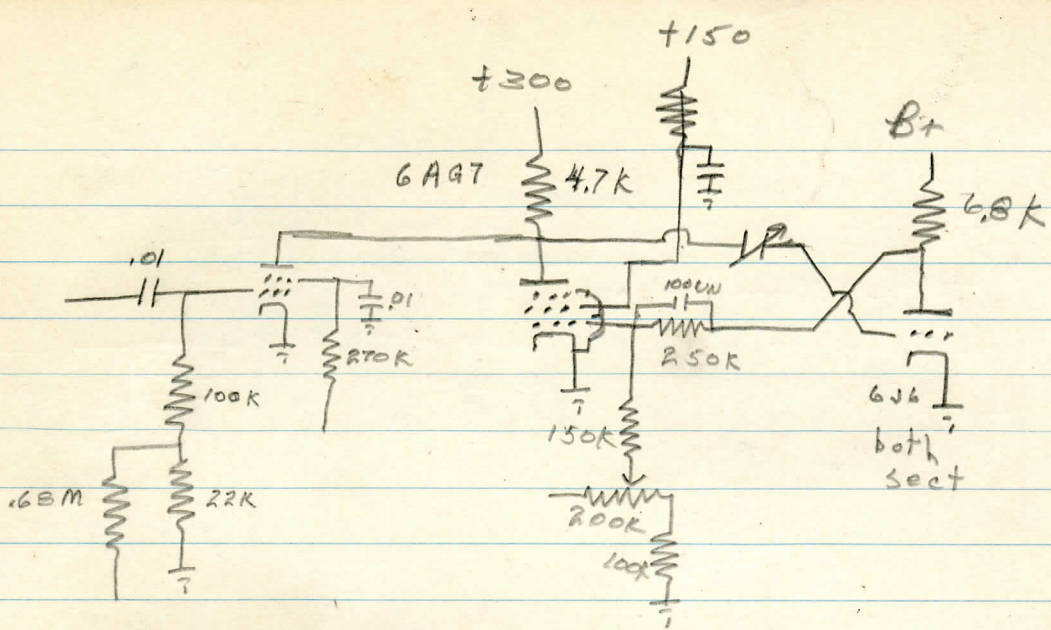

Video Amps -

$\frac{1}{2} \mu\text{sec}$

input - 100 sq. wave

1.5 - 3.5V

Output $\approx 60V$ limited

FTC if desirable - Neg out

Rise Time $\approx 2.2RC$ short


$$m = \frac{L}{RRC}$$


$$m = .25 \text{ no os.}$$

$$m = .41 = 35\% \text{ os.}$$


$$G_{\text{overall}} = \frac{60}{1.5} = 40$$

6AC7 +300 B+ = 12mA

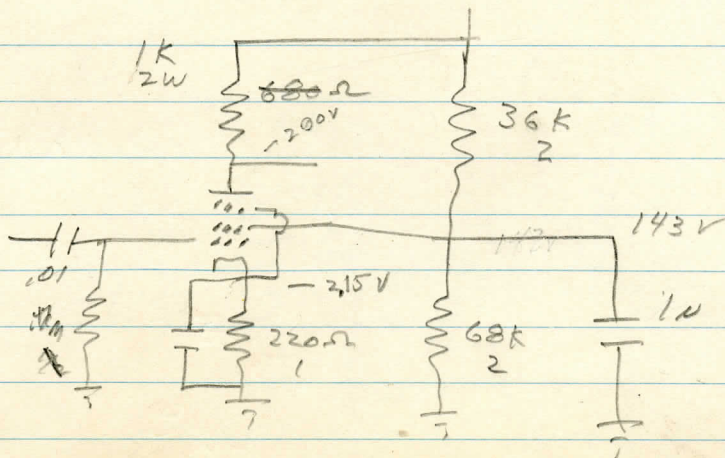


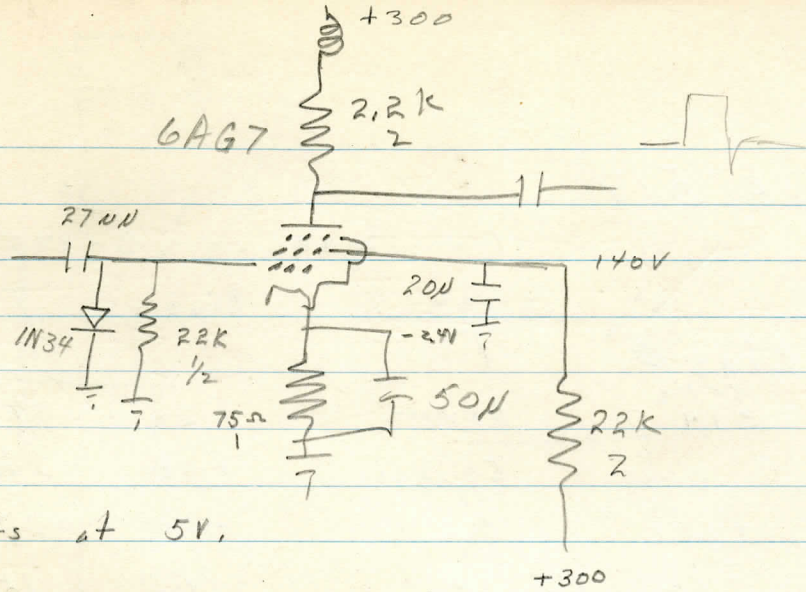

Voltage controlled Flip Flop

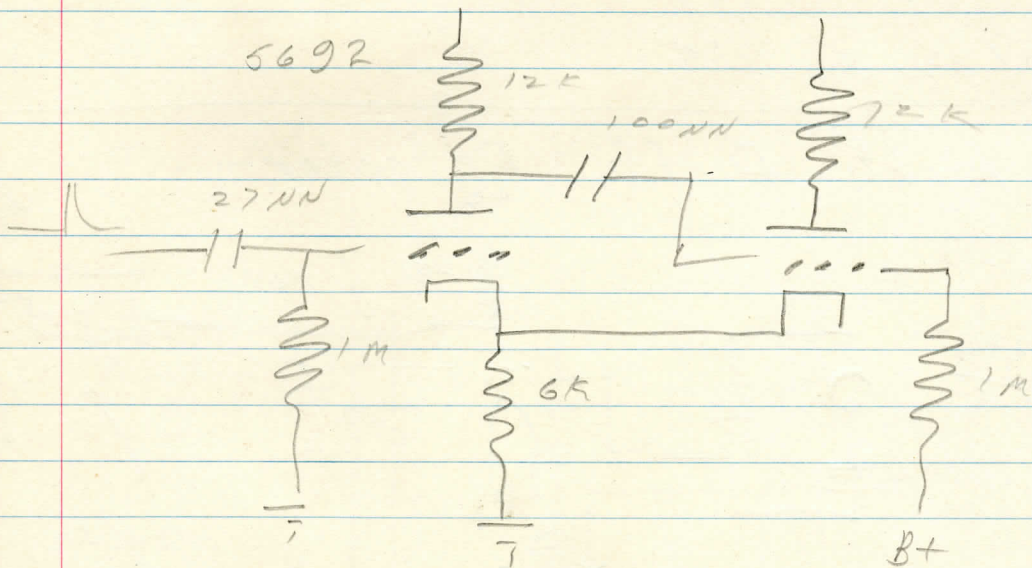

This ckt would not flip when t.

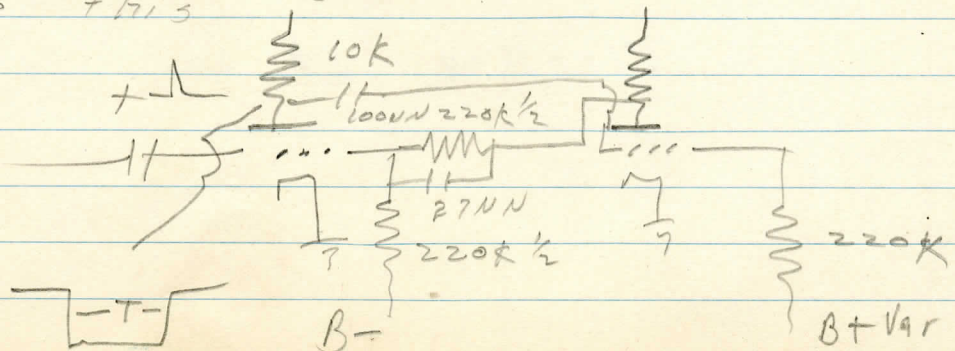

6

4

Tek 517

B + 210

C-175

On

Bias B+Var

T

Bias

T

Volts
-1.4

60 nsec

+25

34

0

55 nsec

+40

28

+1.5

53 "

+60

22

+3.0

56 "

+100

15

+4.5

48 "

+6

46 "

+10



43 "

+15



40 "

Light. Diff. Detector -

$$2 \times 10^{-3} \times 5 \times 10^{-3} = 10$$

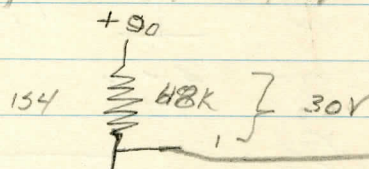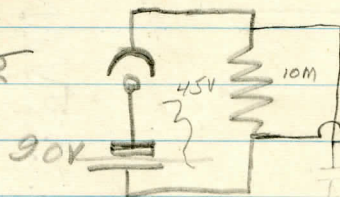
922
P22

+67.5

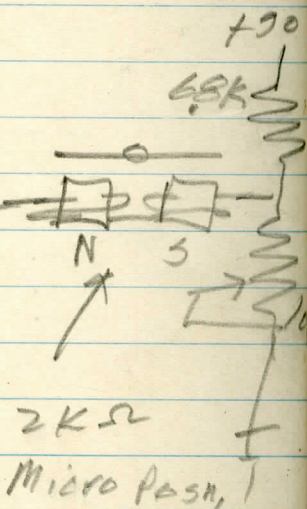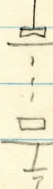

Micro Pash, 1



Worked OK on this CKT

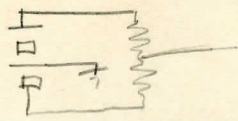


7"



Replace input ckt with this
operated

changed to this

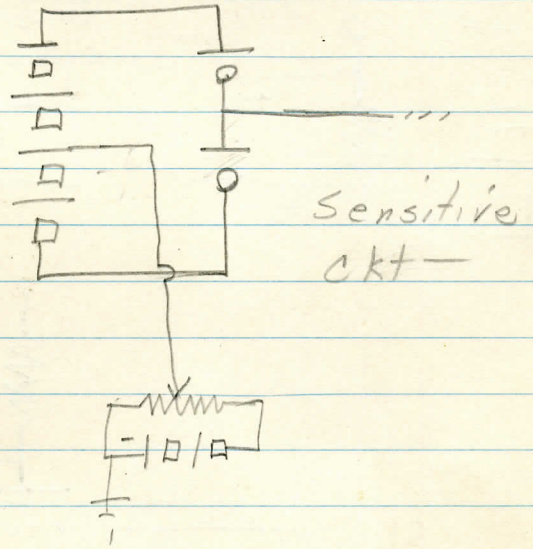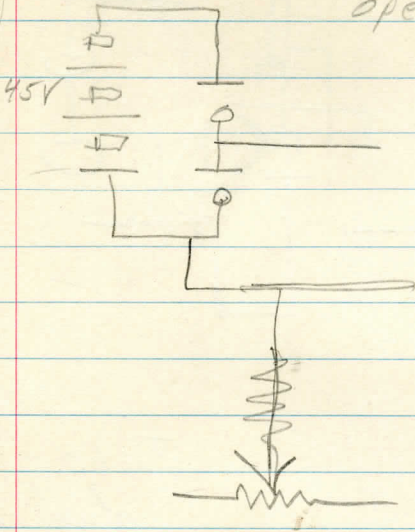


Try this

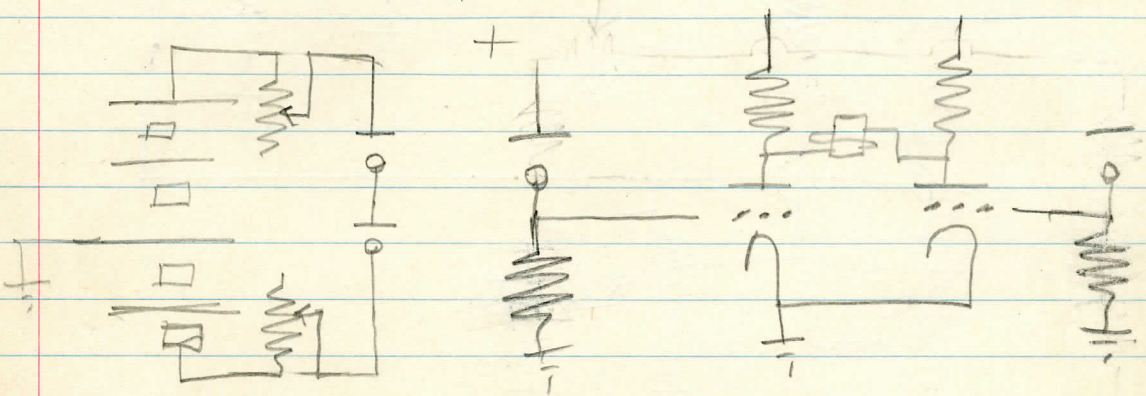

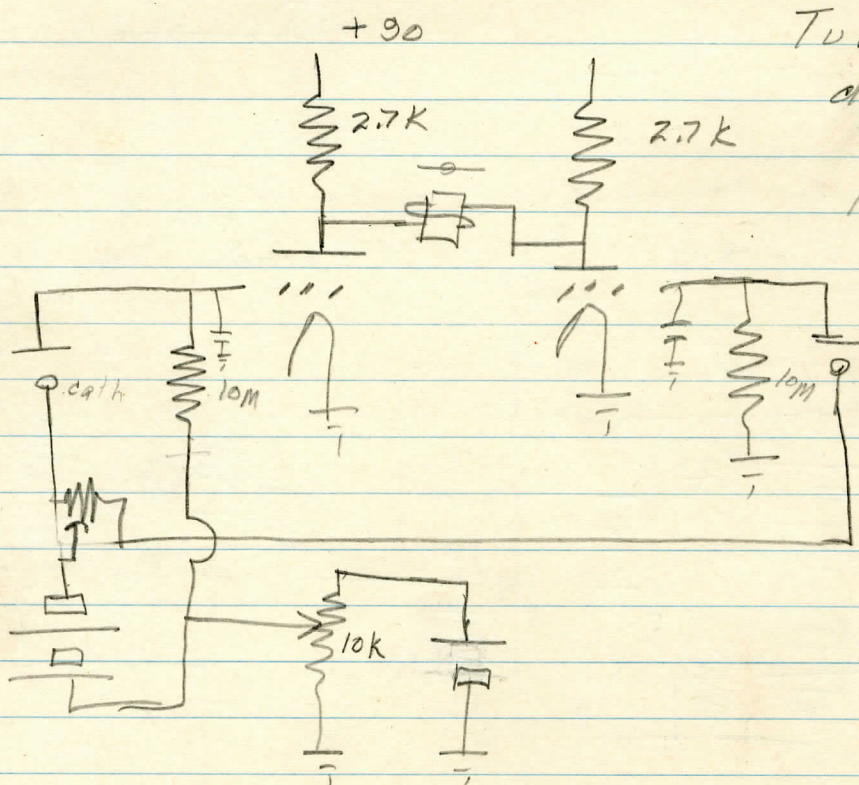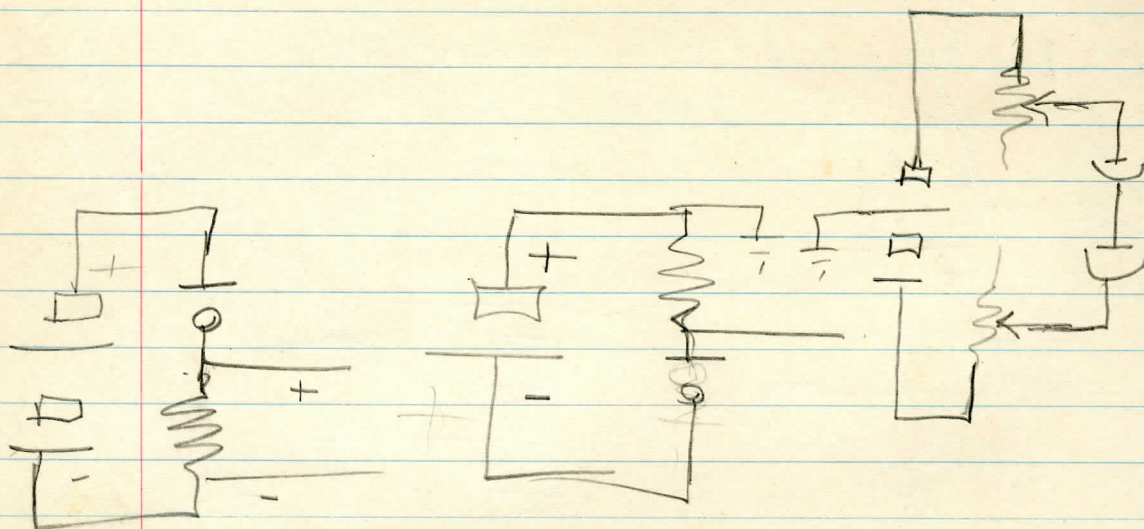

Tube
did not
have
necc-
gm-

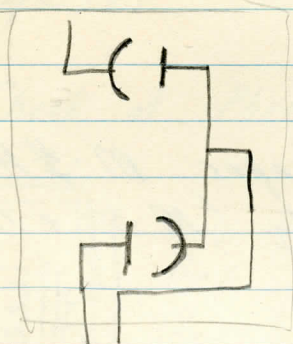

Pulse Generator


Diagrams

- MKI pulse shaper M-~~SA~~ ROFF/

T-7 Pwr Supply (M3 + 750)

9/3/57



Check of Phrenic Integrator -

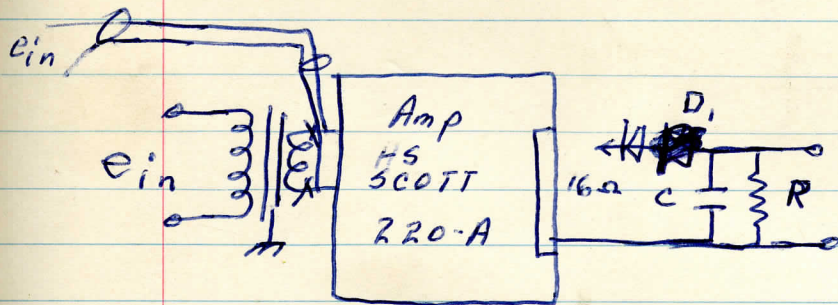


$\bar{c}$ o.p. of GR-1217A directly into direct input of Amp (level adj. = 33 div)

$e_{in} =$


D-1 60 cps

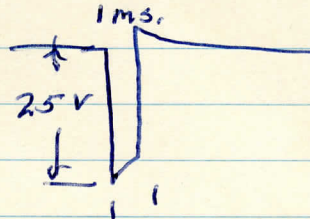
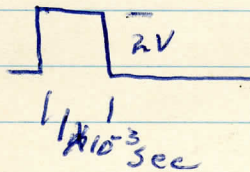


6X4


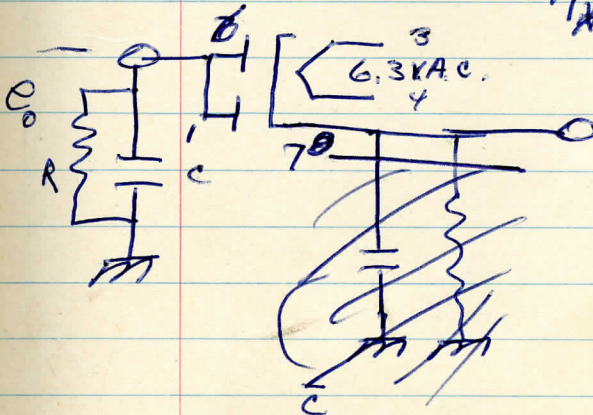


e_{in}
 $R = 5K$
 $C = 1N$

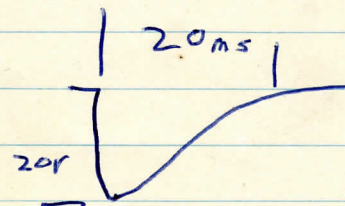

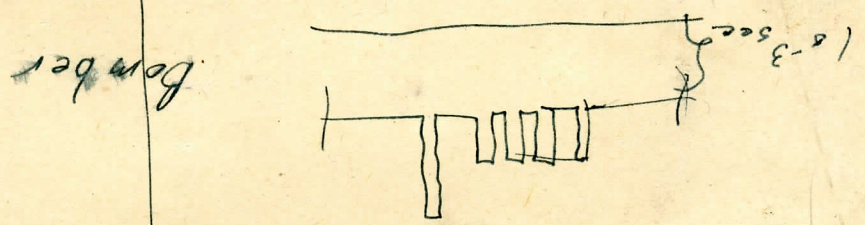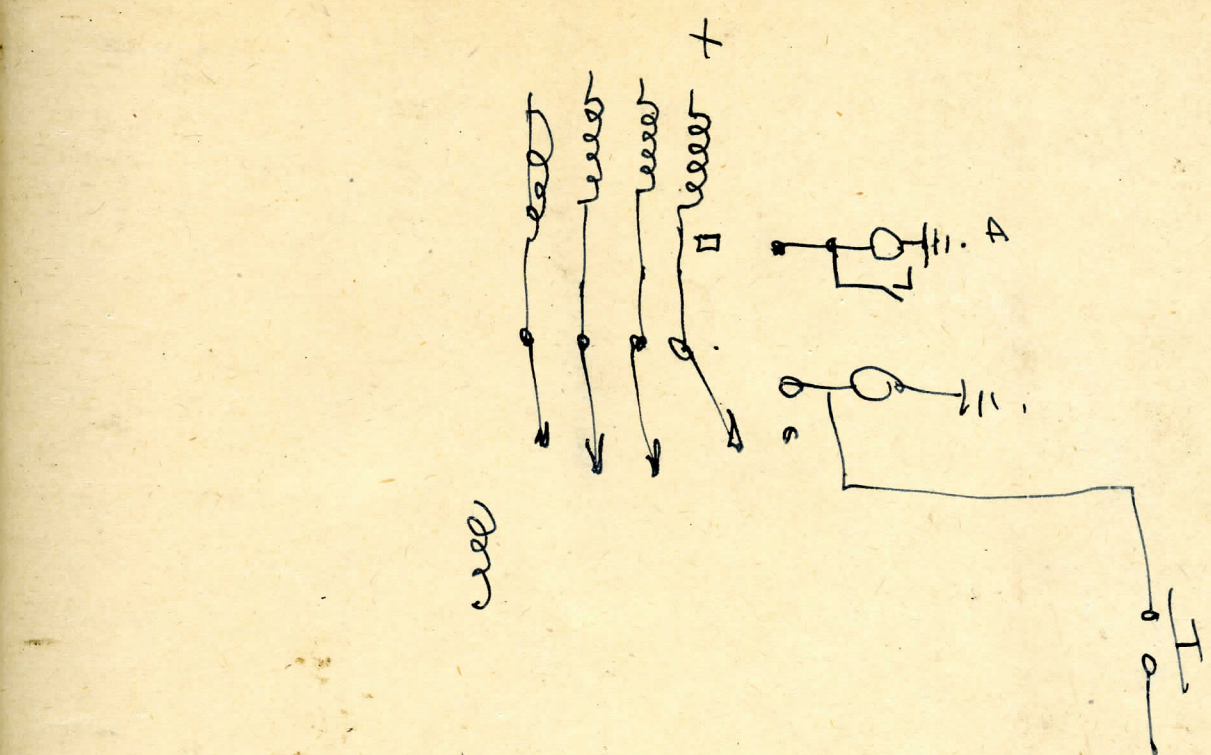

Bomber

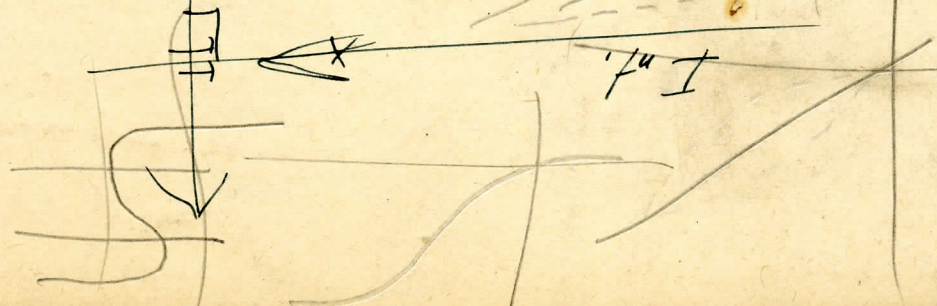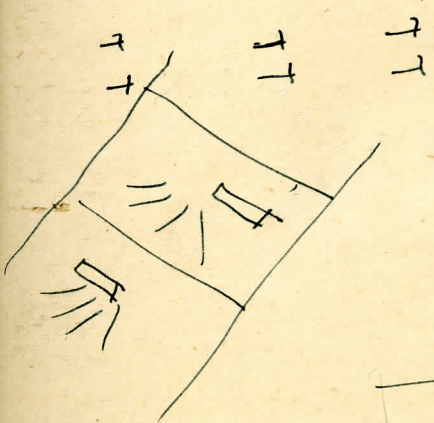

Int.